

ECE 391 – TRANSMISSION LINES AND ELECTROMAGNETIC WAVES

Spring Term 2003

Midterm I

SSN: xxx-xx-_____


(Last name, first name)

Name: _____

Solutions

Exam is closed book, closed notes; one sheet (2 pages) of formulas allowed; 50 minutes. Show all your work on the pages provided. No extra pages (use back if necessary). Read each question very carefully. Maximum number of points for each problem is given in parentheses. Total: 40 points.

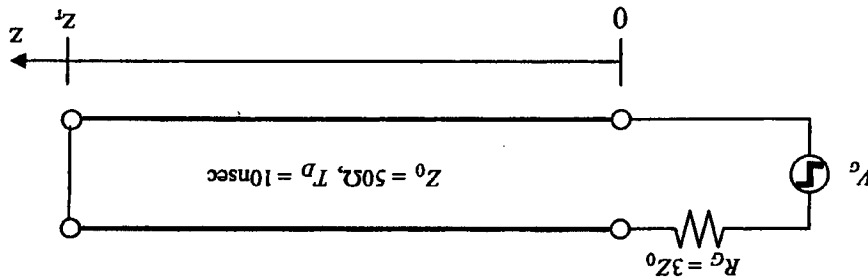1. (25 pts.) At time $t = 0$, a generator with internal resistance $R_G = 3Z_0$ and $V_G = 4$ V is connected to a lossless transmission line with characteristic impedance $Z_0 = 50\Omega$ and delay time $T_D = 10$ nsec. The transmission line is short-circuited at the far end. The propagation velocity on the transmission line is 3×10^8 m/s.



- (a) Determine the length of the line in meters.

$$z_L = V_G \cdot T_D = 3 \times 10^8 \frac{m}{s} \times 10 \times 10^{-9} s = 3m$$

- (b) Determine the voltage reflection coefficients at both ends.

$$\Gamma_L = -1 \text{ (short circuit)}$$

$$\Gamma_G = \frac{3Z_0 - Z_0}{3Z_0 + Z_0} = \frac{2}{4} = \frac{1}{2}$$

- (c) Determine the distributed capacitance and inductance parameters of the transmission line.


$$V_P = \frac{V_G c}{Z_0} = \frac{4 \times 3 \times 10^8}{50} = 2.4 \times 10^{10} \text{ V/m}$$

$$\lambda = \frac{V_P}{Z_0} = \frac{2.4 \times 10^{10}}{50} = 4.8 \times 10^8 \text{ m}$$


$$C = \frac{Z_0 V_P}{\lambda} = \frac{50 \times 2.4 \times 10^{10}}{4.8 \times 10^8} = 2.5 \times 10^{-2} \text{ F/m}$$

$$L = \frac{1}{V_P^2} = \frac{1}{(2.4 \times 10^{10})^2} = 1.736 \times 10^{-22} \text{ H/m}$$

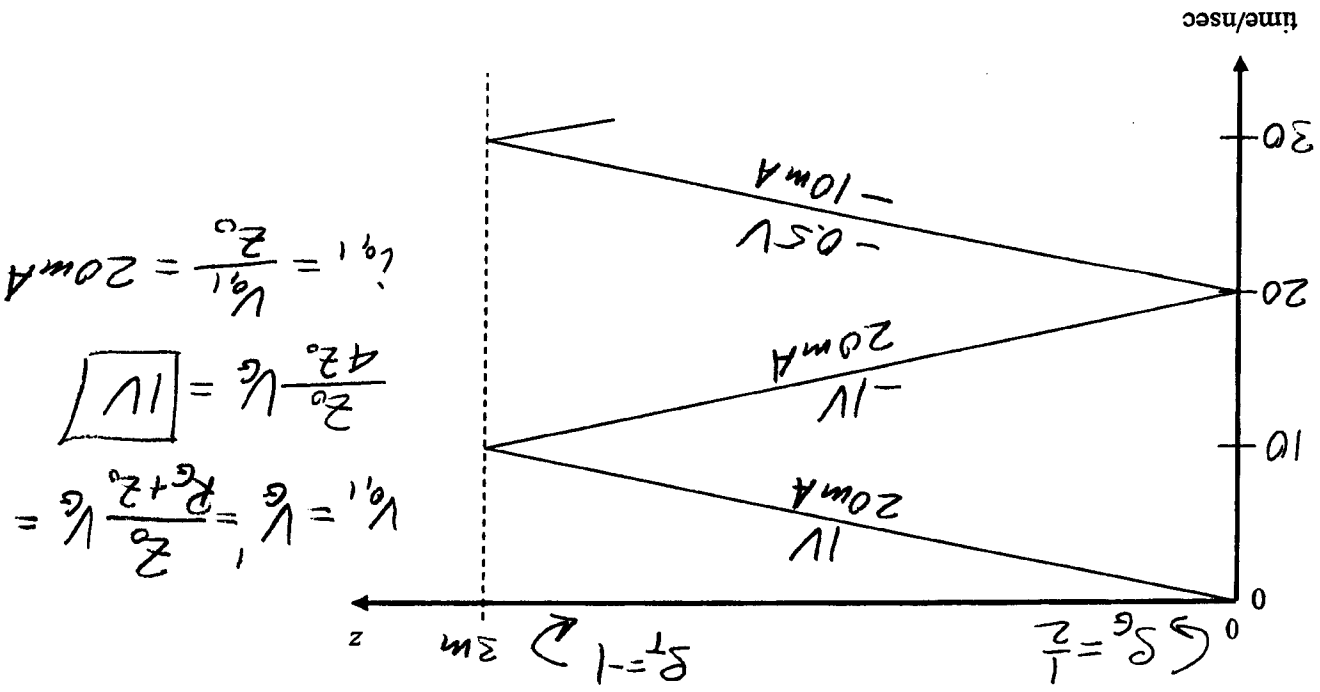(d) Fill in the numerical voltage and current values for the first three wave components and add the time scale and length scale in the lattice diagram shown below.



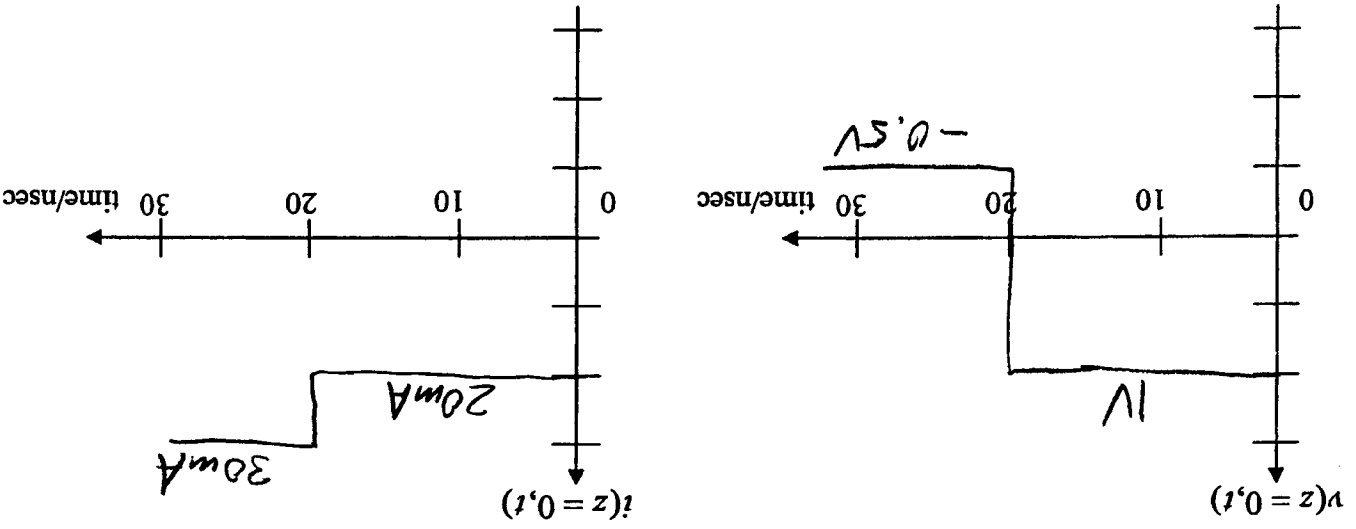(e) Sketch voltage $v(z=0,t)$ and current $i(z=0,t)$ at the beginning of the line ($z=0$) for $0 \leq t \leq 30$ nsec.




(f) Determine $v(z=0)$ and $i(z=0)$ at the input of the line for $t \rightarrow \infty$.

$$V_{\infty} = 0 \text{ (short circuit)}$$

$$I_{\infty} = \frac{V_G}{R_G} = \frac{4V}{150\Omega} = \boxed{26.7 \text{ mA}}$$

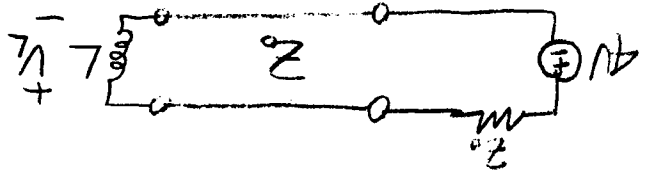(g) Now, the source resistance is changed to $R_G = Z_0 = 50\Omega$ (matched), and the short circuit is replaced by an inductor with inductance $L = 250 \text{ nH}$. Determine and sketch the voltage $v(z=0, t)$ at the input of the line if the source is turned on at time $t = 0$ and no current or voltage exist on the line for $t < 0$.



$$V'_G = \frac{1}{2} V_G = 2V$$

at the inductor: $V_L(t) = 2V_0' e^{-\frac{t}{\tau}}$


$$\tau = \frac{L}{R} = \frac{250 \text{ nH}}{50\Omega} = \boxed{5 \text{ ns}}$$

returning wave: $V_{r1}(t, z=z_0) = V_L(t) - V_{o1}(t, z=z_0)$


$$= \left(2e^{-\frac{t}{\tau}} - 1 \right) V'_G u(t - \tau)$$

at the input: $V_{r1}(t, z=0) = \left[2e^{-\frac{t}{\tau}} - 1 \right] V'_G u(t - 2\tau)$

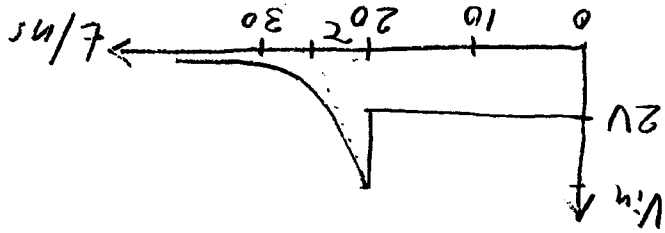total voltage: $V_{in}(t) = V_{o1}(t, z=0) + V_{r1}(t, z=0) = V_{o1}(t) + \left[2e^{-\frac{t}{\tau}} - 1 \right] V'_G u(t - 2\tau)$



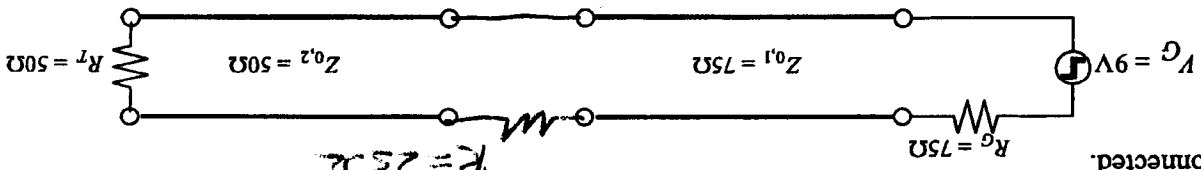2. (15 pts.) Two lossless transmission lines with different characteristic impedances are to be connected.



(a) You have available one resistor R with resistance value of your choice. Show in the figure above how you would connect the two lines and your resistor to eliminate any reflected waves on the two lines. Determine R .

Lines are matched at generator side and termination


$\Rightarrow S_{11} = 0 \Rightarrow$ add series resistor R
 $R + Z_{02} = Z_{01} \Rightarrow R = 25\Omega$

(b) Determine the steady-state voltages at the input of the first line (source side) and at the termination of the second line (R_T) (i.e. for $t \rightarrow \infty$) for the configuration determined in part a.

source side: $V_{\infty} = \frac{R + R_T}{R + R_T + R_G} V_G = 4.5V$

termination: $V_{\infty} = \frac{R_T}{R_T + R + R_G} V_G = 3V$

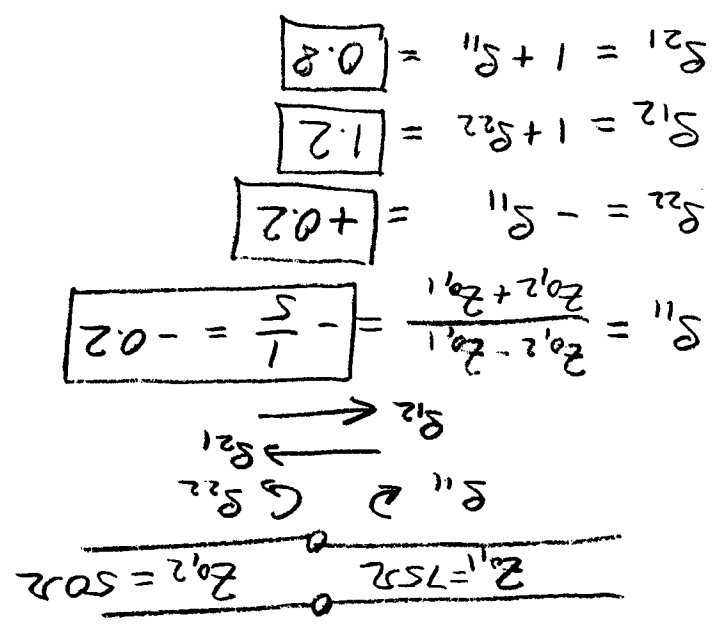(c) Determine the reflection and transmission coefficients $\rho_{11}, \rho_{22}, \rho_{12}, \rho_{21}$ at the junction of the two lines if the lines are directly connected without the additional resistor.




(d) Determine the two reflection coefficients, ρ_{11} and ρ_{22} , at the junction of the two lines when the lines are connected as determined in part a.


$$S_{11} = 0 \quad (\text{as required in part a})$$

$$S_{22} = \frac{Z_{01} + R - Z_{02}}{Z_{01} + R + Z_{02}} = \frac{100 - 50}{100 + 50} = \frac{1}{3}$$

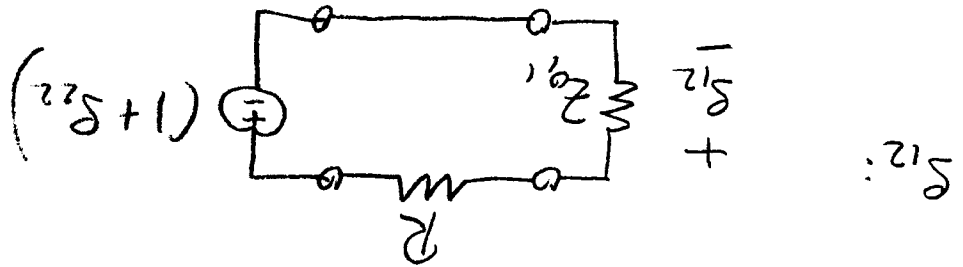(e) Determine the two transmission coefficients, ρ_{12} and ρ_{21} , at the junction of the two lines when the lines are connected as determined in part a.


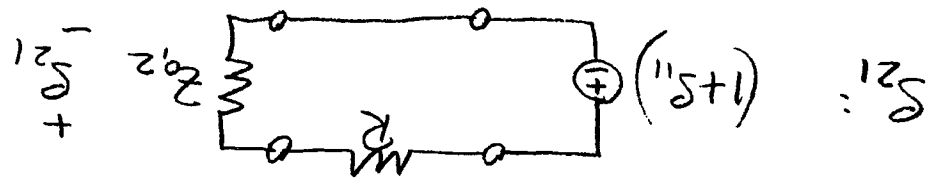
$$S_{12} = \frac{Z_{01}}{R + Z_{01}} (1 + S_{22}) = \frac{100}{75} \cdot \frac{1}{3} = \frac{1}{3}$$



$$S_{21} = \frac{Z_{02}}{R + Z_{02}} (1 + S_{11}) = \frac{50}{100} \cdot \frac{1}{2} = 0.666 \left(\frac{1}{2} \right)$$

ECE 391 - TRANSMISSION LINES AND ELECTROMAGNETIC WAVES

Winter Term 2004

Midterm I

SSN: xxx-xx-_____


(Last name, first name)

Name: _____

Solutions

Exam is closed book, closed notes; one sheet (2 pages) of formulas allowed; 50 minutes. Show all your work on the pages provided. No extra pages (use back if necessary). Read each question very carefully. Maximum number of points for each problem is given in parenthesis. Total: 40 points.

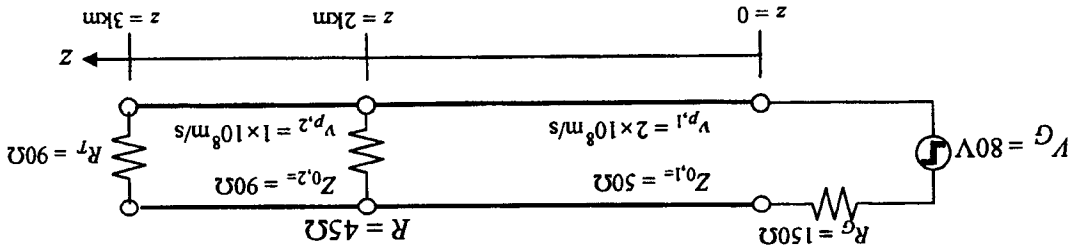1. (20 pts.) Two lossless transmission lines with different characteristic impedances are connected in tandem and excited by a step voltage source as shown below.



(a) Determine the delay times of the two transmission lines.

$$TD_1 = \frac{2 \text{ km}}{2 \times 10^8 \frac{\text{m}}{\text{s}}} = 1 \times 10^{-5} \text{ s} = \boxed{10 \mu\text{sec}}$$

$$TD_2 = \frac{1 \text{ km}}{1 \times 10^8 \frac{\text{m}}{\text{s}}} = 1 \times 10^{-8} \text{ s} = \boxed{10 \text{ nsec}}$$

(b) Determine the voltage and current of the first outgoing wave component traveling on the transmission line connected to the source.

$$V_{o1} = \frac{Z_{01}}{Z_{01} + R_G} V_G = \frac{50}{50 + 150} 80\text{V} = \boxed{20\text{V}}$$


$$I_{o1} = \frac{V_{o1}}{Z_{01}} = \frac{20\text{V}}{50\Omega} = \boxed{400 \text{ mA}}$$

(c) Determine the reflection coefficient at the source and the reflection coefficient at the termination of the second line.

$$\Gamma_G = \frac{R_G - Z_{01}}{R_G + Z_{01}} = \frac{150 - 50}{150 + 50} = \boxed{\frac{2}{1}}$$

$$\Gamma_T = \frac{R_T - Z_{02}}{R_T + Z_{02}} = \frac{90 - 90}{90 + 90} = \boxed{0}$$

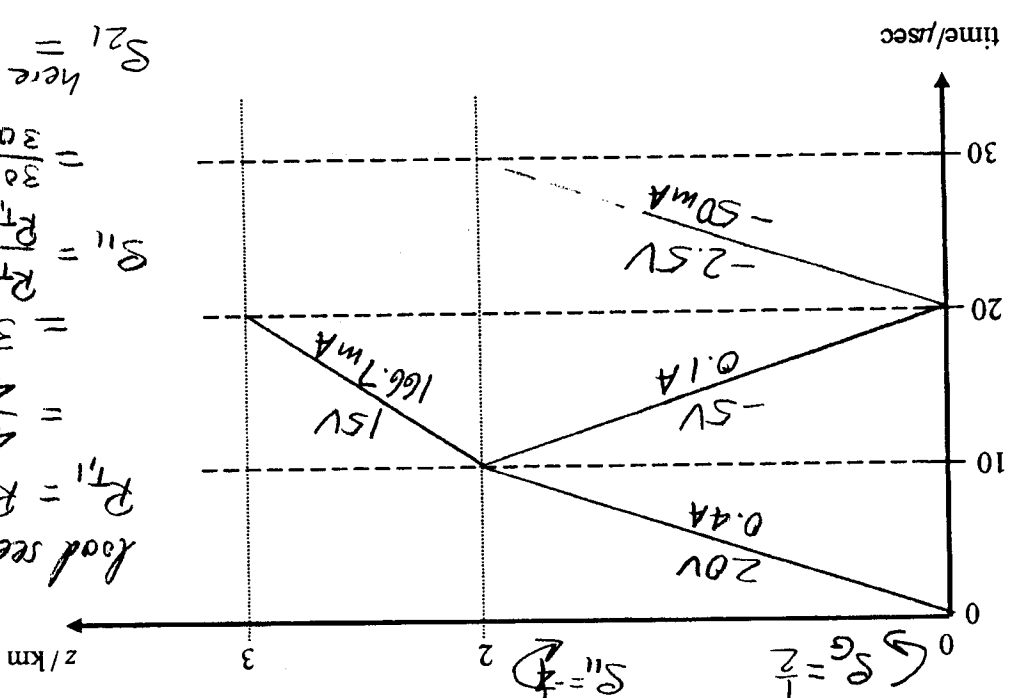(d) Complete the lattice diagram for the system shown below for $0 \leq t \leq 25 \mu\text{sec}$. Give explicit numerical values for the voltage and current of each wave component.




$$R_{T1} = R // Z_{02} = \frac{452 \cdot 902}{452 + 902} = 3052$$

$$S_{11} = \frac{R_{T1} - Z_{01}}{R_{T1} + Z_{01}} = \frac{3052 - 30}{3052 + 30} = -\frac{1}{4}$$

$$S_{21} = \text{here } 1 + S_{11} = \frac{3}{4}$$

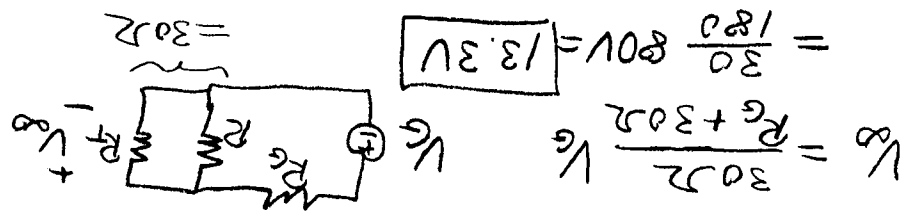(e) Determine the steady-state voltages (i.e. for $t \rightarrow \infty$) at the input of the left cable ($z=0$), at the junction between the two cables ($z=2\text{km}$), and at the end of the second (shorter) cable ($z=3\text{km}$). What is the steady-state current through the load resistor $R_T = 902\Omega$?


for $t \rightarrow \infty, V(z=0) = V(z=2\text{km}) = V(z=3\text{km}) = V_{\infty}$




$$V_{\infty} = \frac{3052}{3052 + 3052} V_G = \frac{180}{30} 80V = 13.3V$$

$$I_{\infty} / R_T = \frac{V_{\infty}}{R_T} = 148.1mA$$

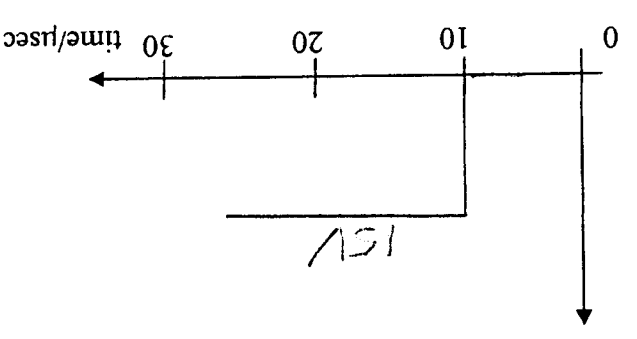(f) Sketch the voltage across the resistor $R = 452\Omega$ at the junction of the two lines for $0 \leq t \leq 25 \mu\text{sec}$ and specify numerical voltage values as appropriate.



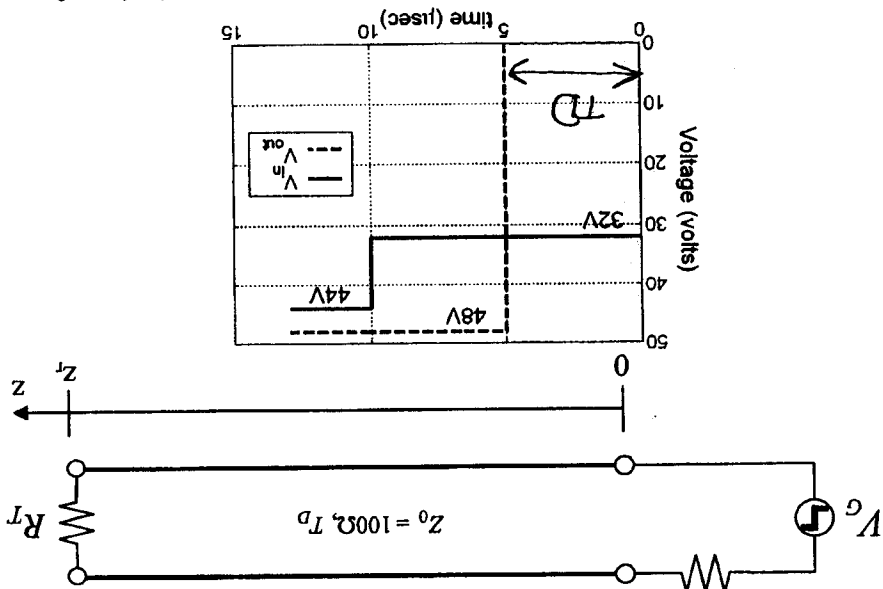2. (20 pts.) At time $t = 0$, a step-function generator with internal resistance R_G and open-circuit voltage V_G is connected to a lossless transmission line of length $z_1 = 500\text{m}$ having characteristic impedance $Z_0 = 100\Omega$. The transmission line is terminated in a resistance R_T at the far end. The voltage waveforms at the input of the line ($z = 0$) and at the end of the line ($z = z_1$) are shown in the figure below for the first 13 μs .



(a) Determine the delay time TD of the transmission line and the velocity of propagation on the line.

$$TD = 5 \mu\text{sec}$$


$$v_p = \frac{TD}{Z_r} = \frac{5 \times 10^{-6}}{1 \times 10^{-8}} = 5 \times 10^8 \frac{\text{m}}{\text{s}}$$

(b) Determine the voltage and the current of the first outgoing wave component.

$$V_{o1} = 32\text{V}$$

$$I_{o1} = \frac{V_{o1}}{Z_0} = 0.32\text{A}$$

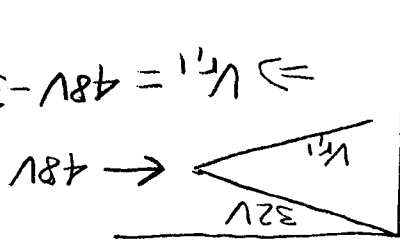
(c) Determine the reflection coefficient ρ_r at the terminating load. (Hint: sketch a lattice diagram.)



$$\Rightarrow V_{r1} = 48\text{V} - 32\text{V} = 16\text{V}$$

$$\rho_r = \frac{V_{r1}}{V_{i1}} = \frac{16\text{V}}{48\text{V}} = 0.5$$

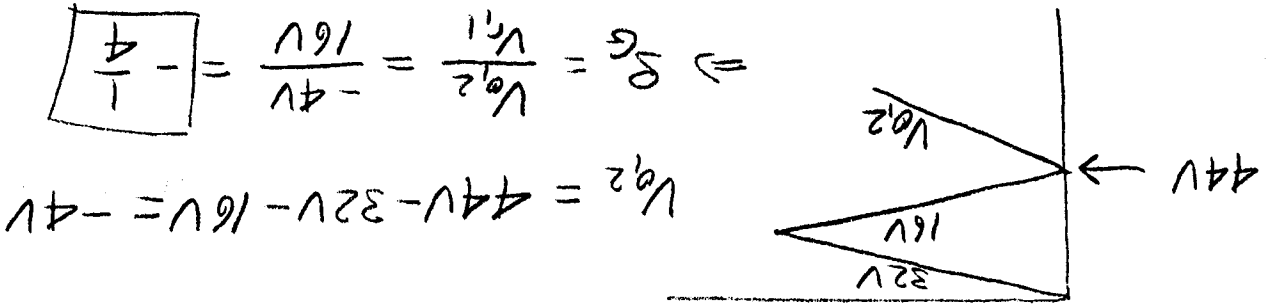(d) Determine the reflection coefficient ρ_G at the generator side. (Hint: sketch a lattice diagram.)





(e) Determine generator resistance R_G , load resistance R_T , and generator voltage V_G .

$$R_G = \frac{1+s_G}{1-s_G} Z_o = \frac{3/4}{5/4} Z_o = 0.6 Z_o = \boxed{60.5 \Omega}$$


$$R_T = \frac{1+s_T}{1-s_T} Z_o = \frac{1.5}{0.5} Z_o = 3 Z_o = \boxed{300.5 \Omega}$$

$$V_G = V_{o1} = \frac{R_G + Z_o}{60 + 100} = 32V = \boxed{51.2V}$$

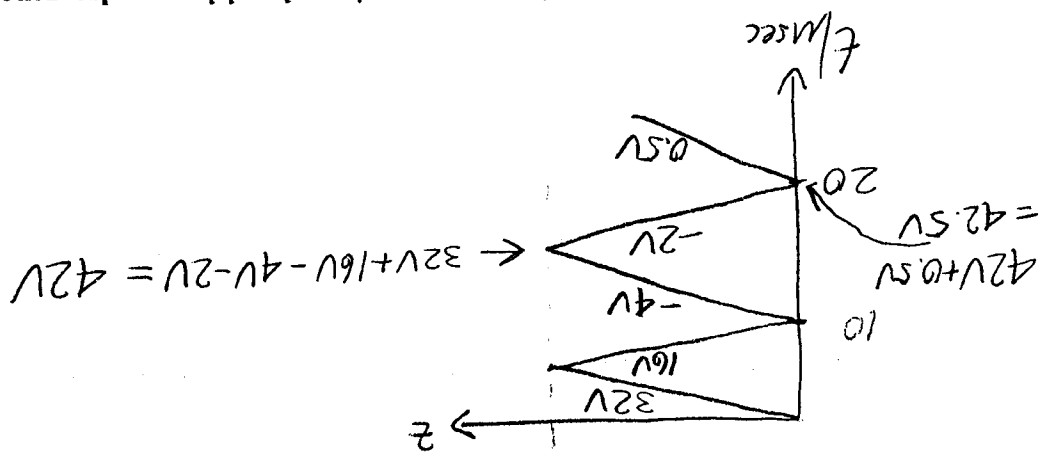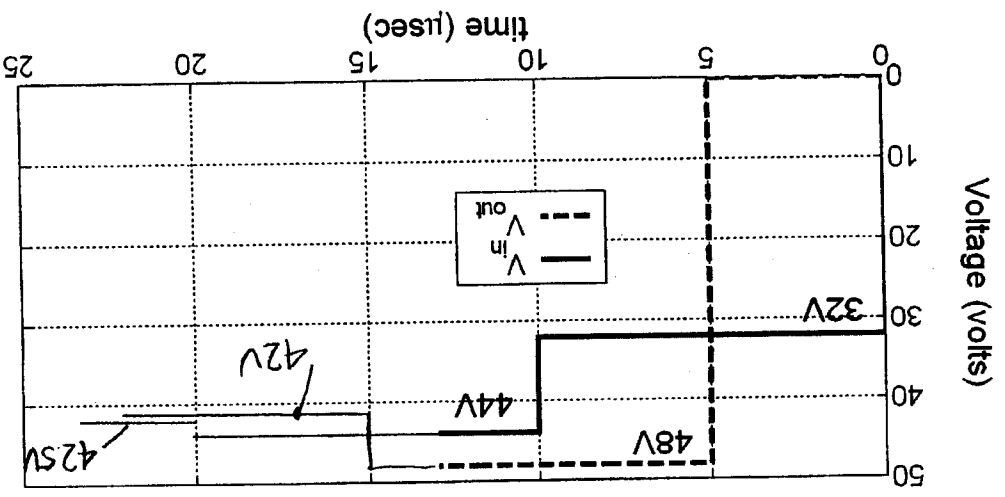(f) Determine and sketch the voltage waveform $v_{in}(t, z=0)$ at the input of the line and $v_{out}(t, z=z_f)$ at the end of the line for $0 \leq t \leq 24 \mu\text{sec}$ and specify the numerical voltage values. (Hint: first sketch a lattice diagram.)



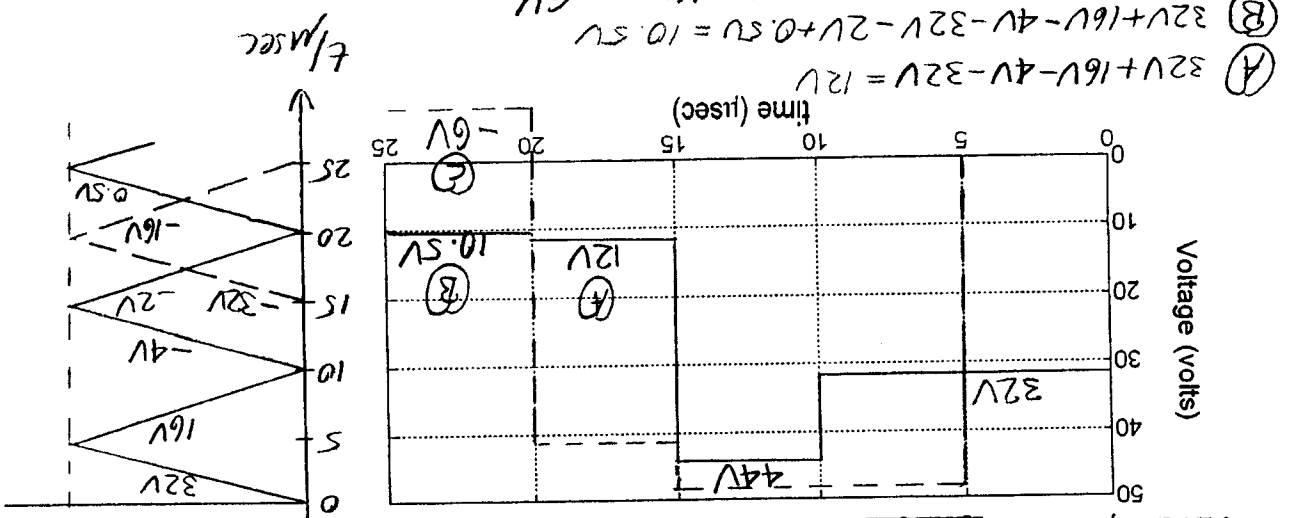(g) Now, the step function generator is replaced by a pulse generator, which at time $t=0$ produces a single rectangular impulse of duration $T=15 \mu\text{sec}$. Sketch the voltage $v_{in}(t, z=0)$ at the input of the line and $v_{out}(t, z=z_f)$ at the end of the line for $0 \leq t \leq 24 \mu\text{sec}$ and specify the numerical voltage values.



- (A) $32V + 16V - 4V - 32V = 12V$
- (B) $32V + 16V - 4V - 32V - 2V + 0.5V = 10.5V$
- (C) $32V + 16V - 4V - 2V - 32V - 16V = -6V$

ECE 391 – TRANSMISSION LINES AND ELECTROMAGNETIC WAVES

Spring Term 2005

Midterm I

Solutions


Name: _____

(Last name, first name)

OSU-ID: _____

Exam is closed book, closed notes; one sheet (2 pages) of formulas allowed; 50 minutes. Show all your work on the pages provided. No extra pages (use back if necessary). Read each question very carefully. Maximum number of points for each problem is given in parenthesis. Total: 40 points.

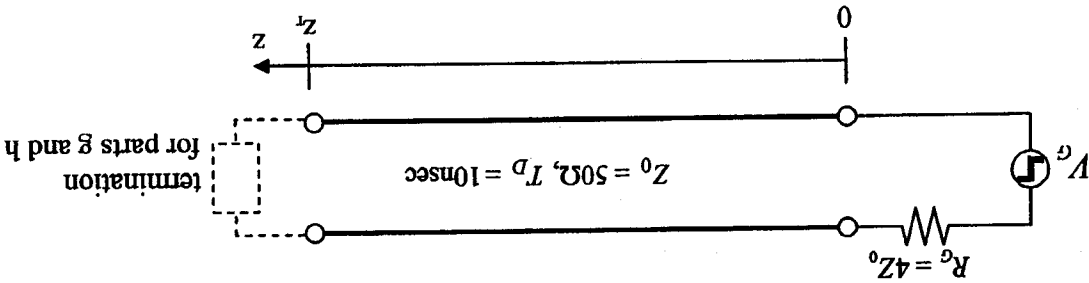1. (25 pts.) At time $t = 0$, a DC generator with internal resistance $R_g = 4Z_0$ and $V_g = 5V$ is connected to a lossless transmission line with characteristic impedance $Z_0 = 50\Omega$ and delay time $T_D = 10\text{nsec}$. The transmission line is open-circuited at the far end. The propagation velocity on the transmission line is $2 \times 10^8 \text{ m/s}$.



- (a) Determine the length of the line in meters.

$$z_T = V_p \cdot T_D = 2 \times 10^8 \frac{\text{m}}{\text{s}} \cdot 10 \times 10^{-9} \text{ s} = \boxed{2 \text{ m}}$$

- (b) Determine the voltage reflection coefficients at both ends.

$$S_G = \frac{R_g - Z_0}{R_g + Z_0} = \frac{4Z_0 - Z_0}{4Z_0 + Z_0} = \frac{4 - 1}{4 + 1} = \frac{3}{5} = \boxed{0.6}$$


$$S_T = \boxed{+1}$$
 (open circuit)

- (c) Determine the distributed capacitance and inductance parameters of the transmission line.
 from $Z_0 = \sqrt{\frac{L}{C}}$ and $V_p = \frac{1}{\sqrt{LC}}$ follows:


$$L = \frac{Z_0}{V_p} = \frac{50 \Omega}{2 \times 10^8 \frac{\text{m}}{\text{s}}} = \boxed{250 \text{ nH/m}}$$

$$C = \frac{1}{Z_0 V_p} = \frac{1}{50 \Omega \times 2 \times 10^8 \frac{\text{m}}{\text{s}}} = \frac{1}{10^{\frac{-10}{\text{m}}}} = \boxed{0.1 \text{ nF/m}}$$

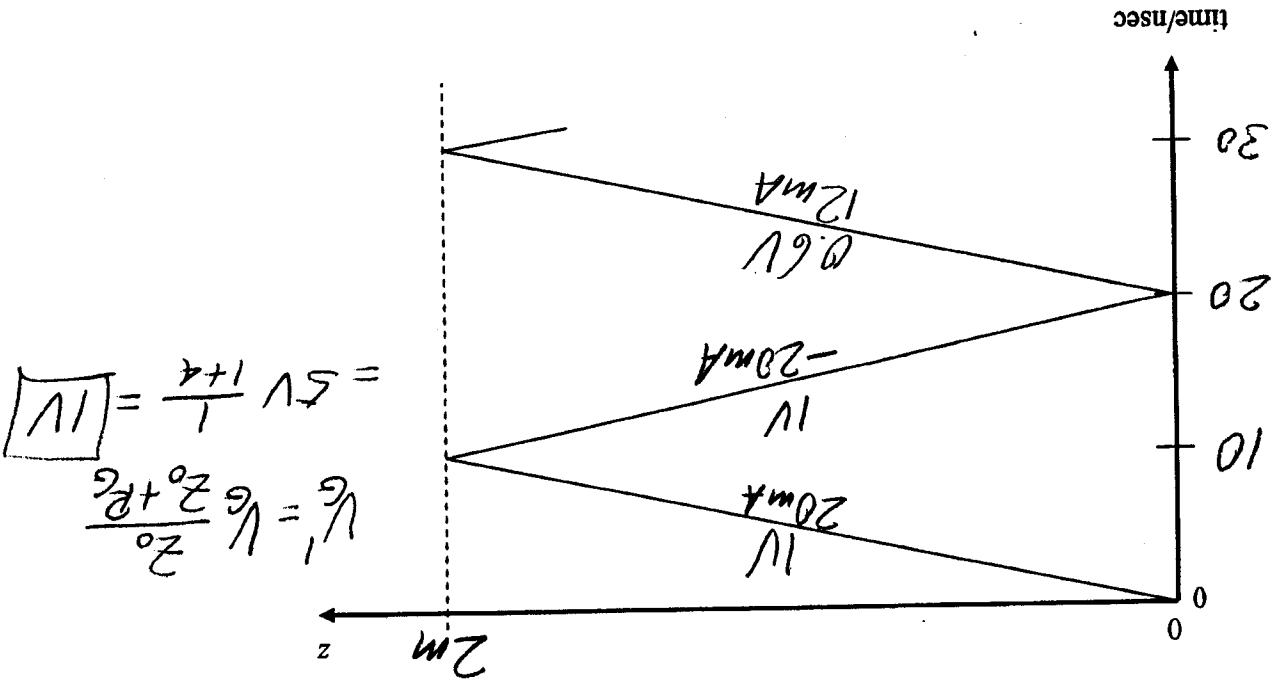(d) Fill in the numerical voltage and current values for the first three wave components and add the time scale and length scale in the lattice diagram shown below.



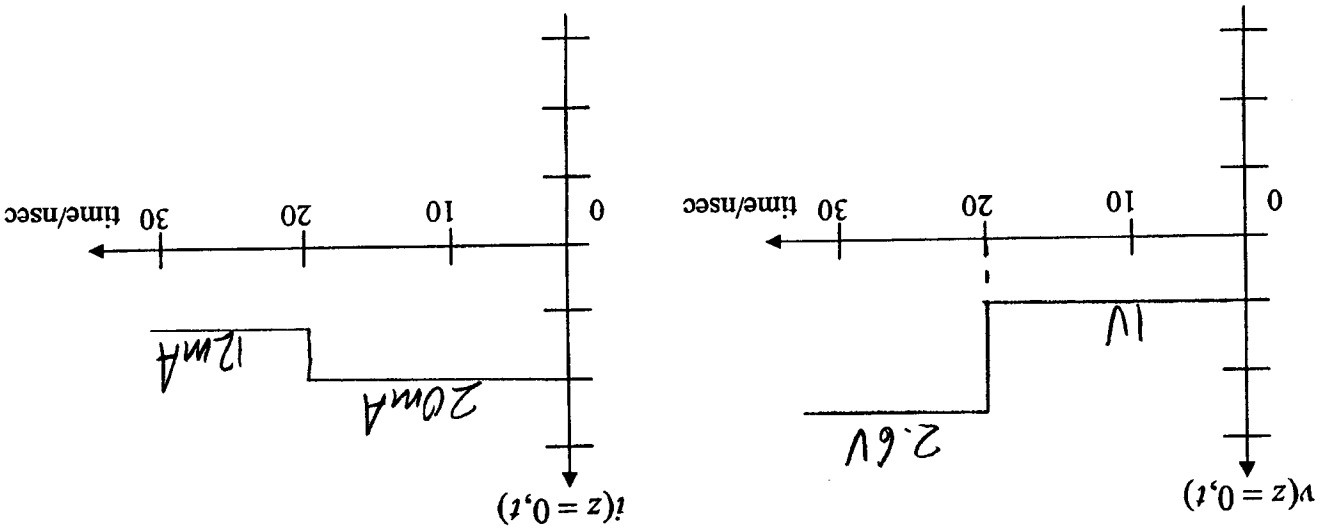
(e) Sketch voltage $v(z=0,t)$ and current $i(z=0,t)$ at the beginning of the line ($z=0$) for $0 \leq t \leq 30$ nsec. (Indicate the specific numerical values on the plots.)



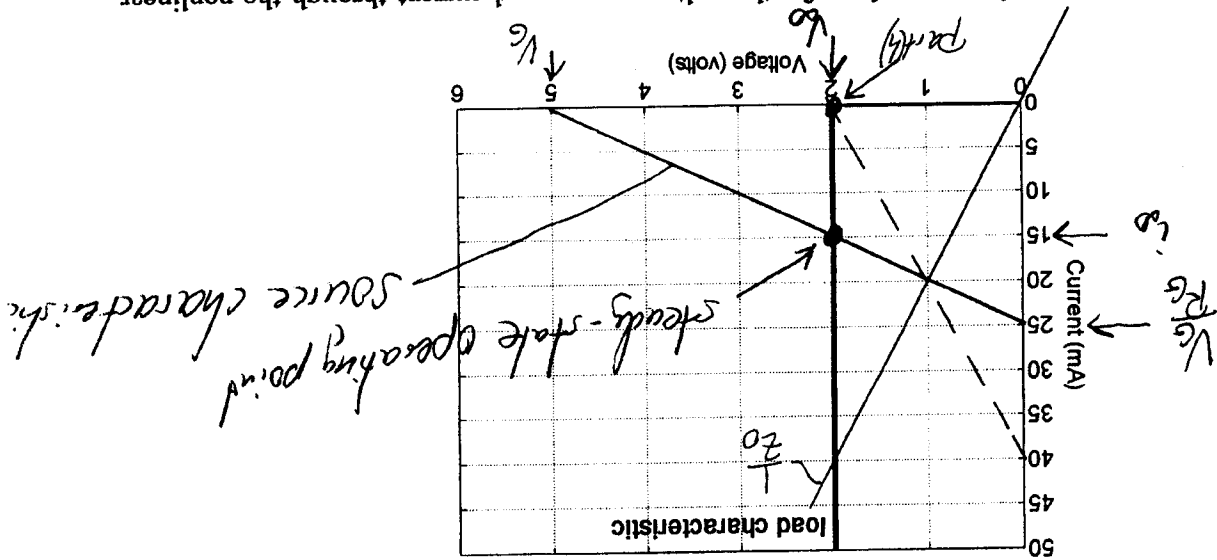(f) Determine $v(z=0)$ and $i(z=0)$ at the input of the line for $t \rightarrow \infty$.

open circuit $\Rightarrow V(t \rightarrow \infty) = V_G = 5V$
 $i(t \rightarrow \infty) = 0$

Now, the line is terminated with a nonlinear load whose I-V characteristic is shown below.



(g) Determine the steady-state values for the voltage across and current through the nonlinear load.

Source characteristic: $V_G = 5V$
 $i_{sc} = \frac{V_G}{R_G} = \frac{5V}{200\Omega} = 25mA$


$\Rightarrow V_D = 2V$
 $i_D = 15mA$

(h) Determine the voltage across and current through the nonlinear load right after the first outgoing wave reaches the load.


- 1) determine outgoing wave values \rightarrow characteristic line through (0) s.t. slope $\frac{1}{z_0}$ at $V = 20mA$
- 2) determine characteristic of the end of the line \rightarrow got through point (1V, 15mA) with slope $= -\frac{z_0}{1}$

$\Rightarrow V_{load} = 2V$
 $i_{load} = 0$
 (from its section with load characteristic)

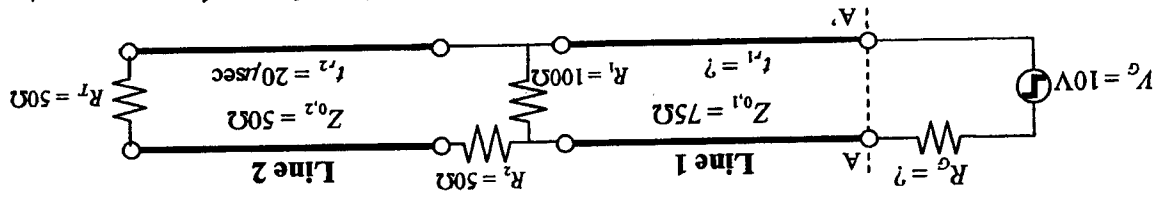2. (15 pts.) Two lossless transmission lines with different characteristic impedances are connected through a network consisting of two resistors, as shown below. The delay time of the first line is unknown, whereas the delay time of the second line is 20 μ sec.



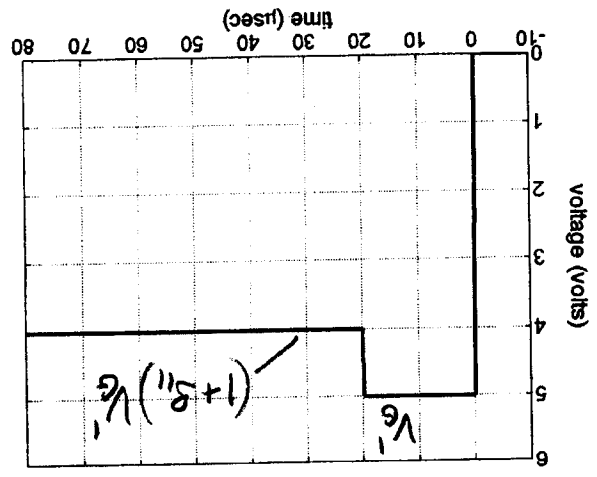At time $t = 0$, a 10V battery is connected to the input of line 1 through an unknown generator resistance R_g . The voltage as a function of time shown below is observed on an oscilloscope connected at the input terminals of line 1 (at A-A').



(a) Determine the delay time t_1 of line 1.
 from graph: $2t_1 = 20 \mu\text{sec} \Rightarrow t_1 = 10 \mu\text{sec}$



(b) Determine the generator resistance R_g .
 $V_g = 10\text{V}$ and $V_g' = 5\text{V}$ (from graph)
 $\Rightarrow R_g = Z_0 = 75\Omega$

(c) Determine the reflection coefficient ρ_{11} at the junction between the two lines.
 from graph: $S_{11} = \frac{5\text{V}}{-1\text{V}} = -0.2$


$$S_{11} = \frac{50 - 75}{50 + 75} = -0.2$$

(d) Determine the transmission coefficient ρ_{21} at the junction between the two lines.
 voltage divider
 $Z_{01} = (1 + S_{11}) \frac{Z_{02}}{2} = \frac{1}{2}(1 + S_{11}) \frac{Z_{02}}{Z_{02}} = \frac{1}{2}(1 + S_{11})$
 $S_{21} = \frac{5\text{V}}{10\text{V}} = 0.5$

$$S_{21} = \frac{5}{10} = 0.5$$

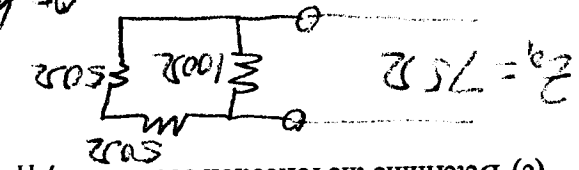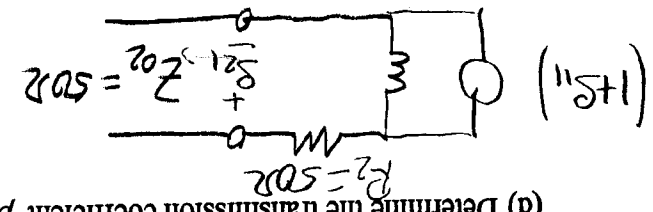

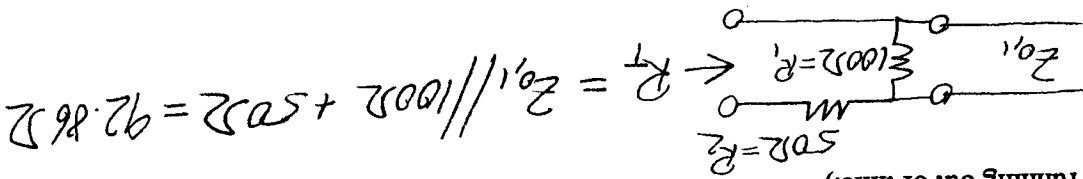
(e) Determine the reflection coefficient p_{22} and the transmission coefficient p_{12} at the junction between the two lines. (Recommendation: Skip to the next part if you are unsure and you are running out of time.)




$$S_{22} = \frac{R_T - Z_{02}}{R_T + Z_{02}} = \boxed{0.3}$$

$$S_{12} = \frac{R_L || Z_{01}}{R_L || Z_{01} + R_T} (1 + S_{22}) = \dots = \boxed{0.6}$$

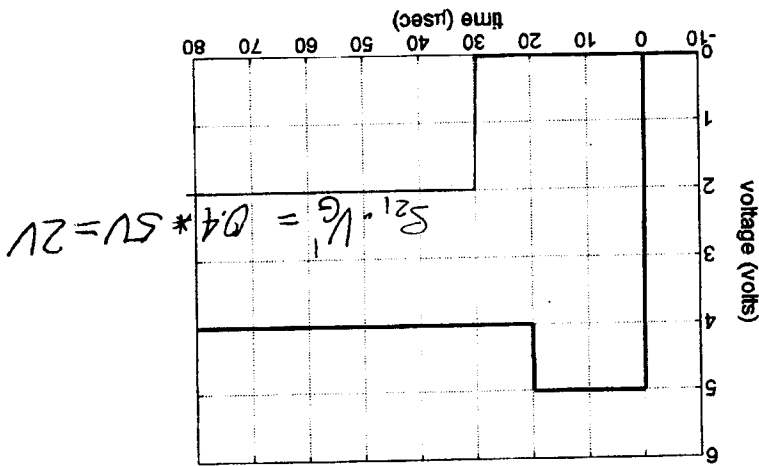(f) Add the voltage waveform across the terminating resistor R_T for $-10 \leq t \leq 80 \mu\text{sec}$ to the plot of the voltage at A-A' shown again below.



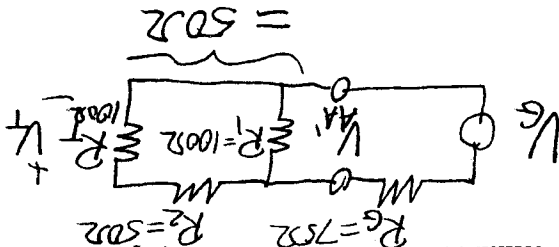(g) Determine the steady-state voltages at the input of the first line (A-A') and across the termination of the second line (R_T) (i.e. for $t \rightarrow \infty$).



$$V_{A-A'}(t \rightarrow \infty) = \frac{50}{50 + 75 + 100} V_G = \frac{50}{225} V_G = \frac{5}{2} V_G = \boxed{4V}$$

$$V_T(t \rightarrow \infty) = \frac{R_T}{R_T + R_L} V_{A-A'}(t \rightarrow \infty) = \frac{50}{150} \cdot 4V = \frac{2}{3} \cdot 4V = \boxed{2.67V}$$

(compare with (f)!) ↓

ECE 391 – TRANSMISSION LINES AND ELECTROMAGNETIC WAVES


Spring Term 2005

Midterm II

Name: Solutions Student ID _____

Exam is closed book, closed notes; one sheet (2 pages) of formulas allowed; 50 minutes. Show all your work on the pages provided. No extra pages (use back if necessary). Read each question very carefully. Maximum number of points for each problem is given in parenthesis. Total: 40 points.

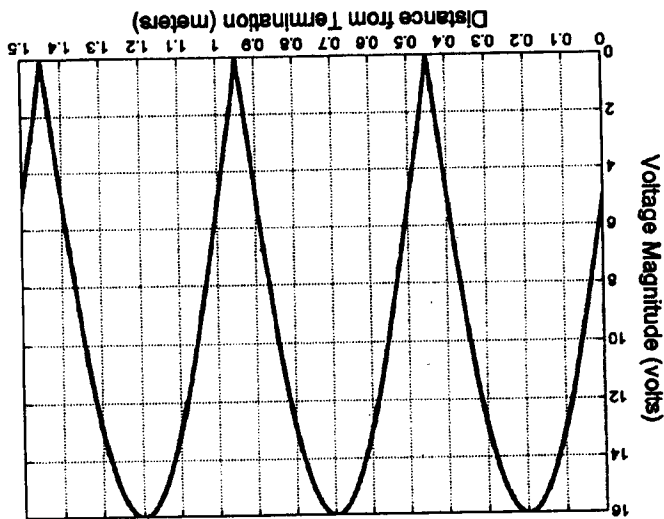1. (12 pts.) A 50Ω coaxial transmission line (filled with air) is terminated in an unknown load impedance Z_T . The voltage standing-wave on the transmission line measured in meters from the termination is shown below.



(a) What is the standing-wave ratio on the line terminated in the unknown load impedance Z_T ?

$$SWR = \frac{V_{max}}{V_{min}} = \infty$$

(b) Determine the wavelength on the line.
 distance between adjacent maxima or minima = $\frac{\lambda}{2}$
 here: $\frac{\lambda}{2} = (0.7 - 0.2) \text{ m} = 0.5 \text{ m}$

$$\lambda = 1 \text{ m}$$

$$z_T = j0.325 \Rightarrow z_T = z_0 = j16.25 \Omega$$

or from Smith chart

$$z_T = z_0 \frac{1+k}{1-k} = j16.25 \Omega$$

(e) Determine the load impedance Z_T in ohms. (An optional Smith Chart is attached at the end.)

or: from Smith chart
 1) V_{max} at $\phi = 0$ ($\Rightarrow 0.25 \lambda$ "forward load" scale)
 2) go 0.28 toward load $\rightarrow 0.45$
 3) read off $\theta_R = 144^\circ$

$$\Rightarrow \theta_R = 2 * 72^\circ = 144^\circ$$

$$\theta_R = \text{shift of maximum voltage} = \frac{0.2\lambda}{\lambda} 360^\circ = 72^\circ$$

$$SWR = \infty \Rightarrow |K| = 1$$

$$K = |K| e^{j\theta_K}$$

(d) Determine the reflection coefficient at the termination (magnitude and phase).

$$\text{or } V_m^+ = \frac{1}{2} (V_{max} + V_{min})$$

$$|K| = 1 \Rightarrow V_m^+ = \frac{1}{2} V_{max} = 8V$$

(c) Determine the voltage amplitude $|V_m^+|$ of the incident wave.

2. (20 pts.) A lossless transmission line of characteristic impedance $Z_0 = 100\Omega$ is terminated in a complex impedance $Z_T = R_T + jX_T$. The normalized load impedance $z_T = Z_T/Z_0$ is specified on the attached Smith Chart. Use the attached Smith Chart to solve all of the following problems. Show all your work on the Smith Chart to get points!

(a) Determine the normalized load impedance $z_T = Z_T/Z_0$ and give the terminating impedance $Z_T = R_T + jX_T$ in ohms.

$$z_T = 0.5 - j0.6 \Rightarrow Z_T = z_T \cdot Z_0 = (50 - j60)\Omega$$

(b) Determine the corresponding normalized load admittance and load admittance in siemens (clearly show your work on the Smith chart!).

from Smith chart

$$y_T = 0.825 + j0.975 \Rightarrow Y_T = \frac{y_T}{Z_0} = (0.00825 + j0.00975) S$$

just for comparison (with calculator): $Y_T = 0.0082 + j0.0098 S$

(c) Determine the reflection coefficient (magnitude and phase in degrees) at the termination.

from Smith chart:

$$|K| = 0.48$$

$$\theta_K = -108^\circ$$

(d) Determine the voltage standing-wave ratio on the line.
 note: if you determine θ_K from Y_T , you have to include the change from K to $-K$ i.e. add 180°

from Smith chart:

$$SWR = 2.8$$

(e) Determine the distance d_{min} to the nearest current minimum from the termination.

current minimum occurs at $\phi = 0$
 \Rightarrow voltage maximum at $\phi = 0$
 \Rightarrow go from 0.4 to 0.5 to 0.25

$$d_{min} = 0.5 - 0.4 + 0.25 = 0.35 \lambda$$

(f) Determine the input impedance $Z_{in}(d_1) = R_{in} + jX_{in}$ in ohms at distance $d_1 = 1.228 \lambda$ from the termination.

go from 0.4 to 0.4 + 1.228 = 1.628 \Rightarrow 0.128
 on "towards generator" scale
 lead off: $Z_{in} \approx 0.63 + j0.82 \Rightarrow Z_{in} = Z_0 \cdot Z = (63 + j82) \cdot 5$

(g) A resistor $R_s = 70 \Omega$ is inserted in series at distance $d_1 = 1.228 \lambda$ from the termination. Determine the new standing-wave ratio on the line for $d > d_1$ (i.e., on the line segment closer to the generator).

add R_s in series:

- 1) normalize $r_s = \frac{R_s}{Z_0} = 0.7$
- 2) add $r_s = 0.7$ to $r_{in} = 0.63$
- 3) new $r = r_s + r_{in} = 1.33$
- 4) x_{in} remains unchanged
- 5) draw $|r| = \text{const}$ circle through new impedance
- 6) lead off new SWR

\Rightarrow $SWR = 2.1$

(h) Now, assume that the operating frequency is increased by 20% and the terminating impedance remains unchanged. Determine the new input impedance at distance d_1 from the termination without the series connected resistor. Hint: the physical distance d remains unchanged.

increase in f by factor 1.2 means
 decrease in λ by factor $\frac{1}{1.2}$ and
 increase in $\frac{d}{\lambda}$ by factor 1.2


new $\frac{d}{\lambda} = 1.228 * 1.2 = 1.4736 \approx 1.474$

on "towards generator" scale "go from 0.4 to 0.4 + 1.474 = 1.874 \Rightarrow 0.374


\Rightarrow lead off $Z_{in} = 0.63 - j0.78$
 $Z_{in} = 63 - j78 \Omega$

IMPEDANCE OR ADMITTANCE COORDINATES

Smith chart for problem 2

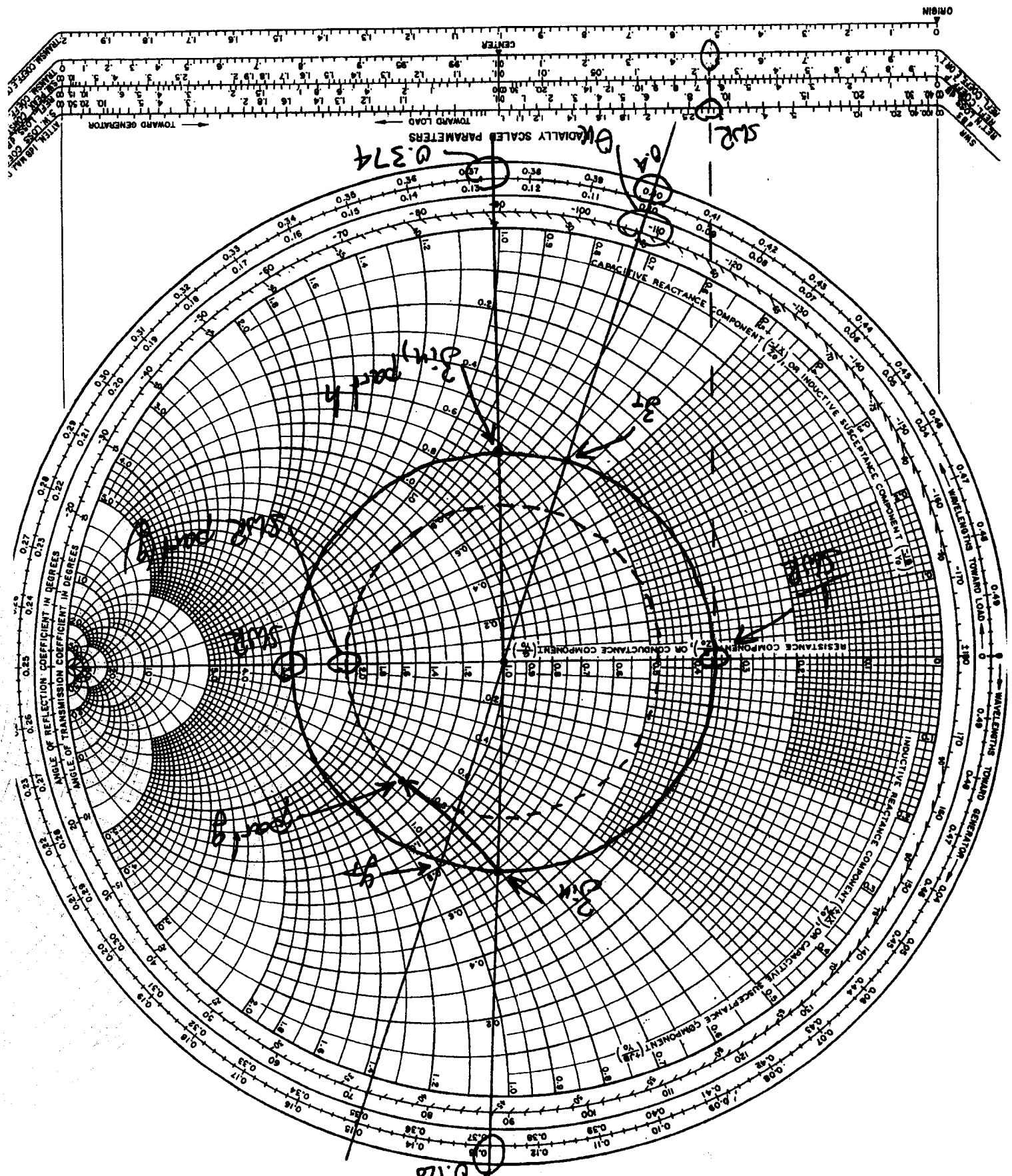

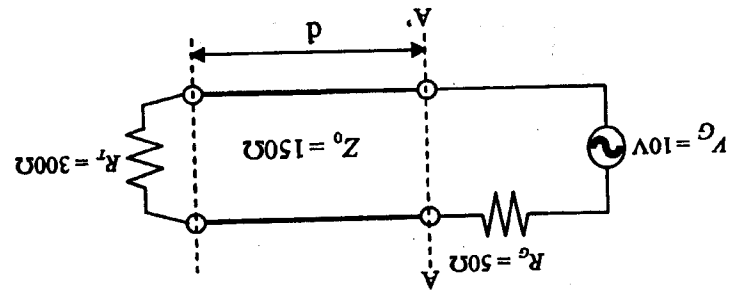3. (8 pts.) A source with a 50Ω generator resistance is connected to a resistive load $R_T = 300\Omega$ through a section of lossless transmission line of length $d = 2$ meters and characteristic impedance $Z_0 = 150\Omega$. The propagation velocity on the line is $v_p = 2 \times 10^8$ m/s.




(a) What is the voltage standing-wave ratio on the line?
 $SWR = \frac{R_T}{Z_0} = 2$ (since $R_T > Z_0$)

(b) Determine the lowest frequency $f = f_0 > 0$ at which the generator sees a purely resistive load impedance at terminals A-A.

for $d = \frac{\lambda}{2}$ line transforms from real to real
 $\Rightarrow \lambda = 4d = 8m$
 $f_0 = \frac{v_p}{\lambda} = \frac{2 \times 10^8}{8m} = 25 \text{ MHz}$

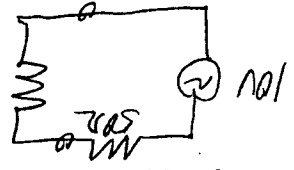(c) Determine the average power dissipated in the terminating resistance R_T at frequency $f = f_0$ determined in part b.



$$Z_{in} = \frac{Z_0^2}{R_T} = \frac{(150\Omega)^2}{300\Omega} = 75\Omega$$

$$V_{in} = 10V \frac{75}{75 + 50} = 6V$$


$$P_{avg} = \frac{1}{2} \frac{V_{in}^2}{R_T} = \frac{1}{2} \frac{(6V)^2}{75\Omega} = 0.24W$$

(d) Determine the average power dissipated in the terminating resistance R_T at frequency $f = 2f_0$.

$$d = \frac{\lambda}{2} \Rightarrow R_{in} = 300\Omega$$

$$V_{in} = 10V \frac{300}{300 + 50} = 8.57V$$
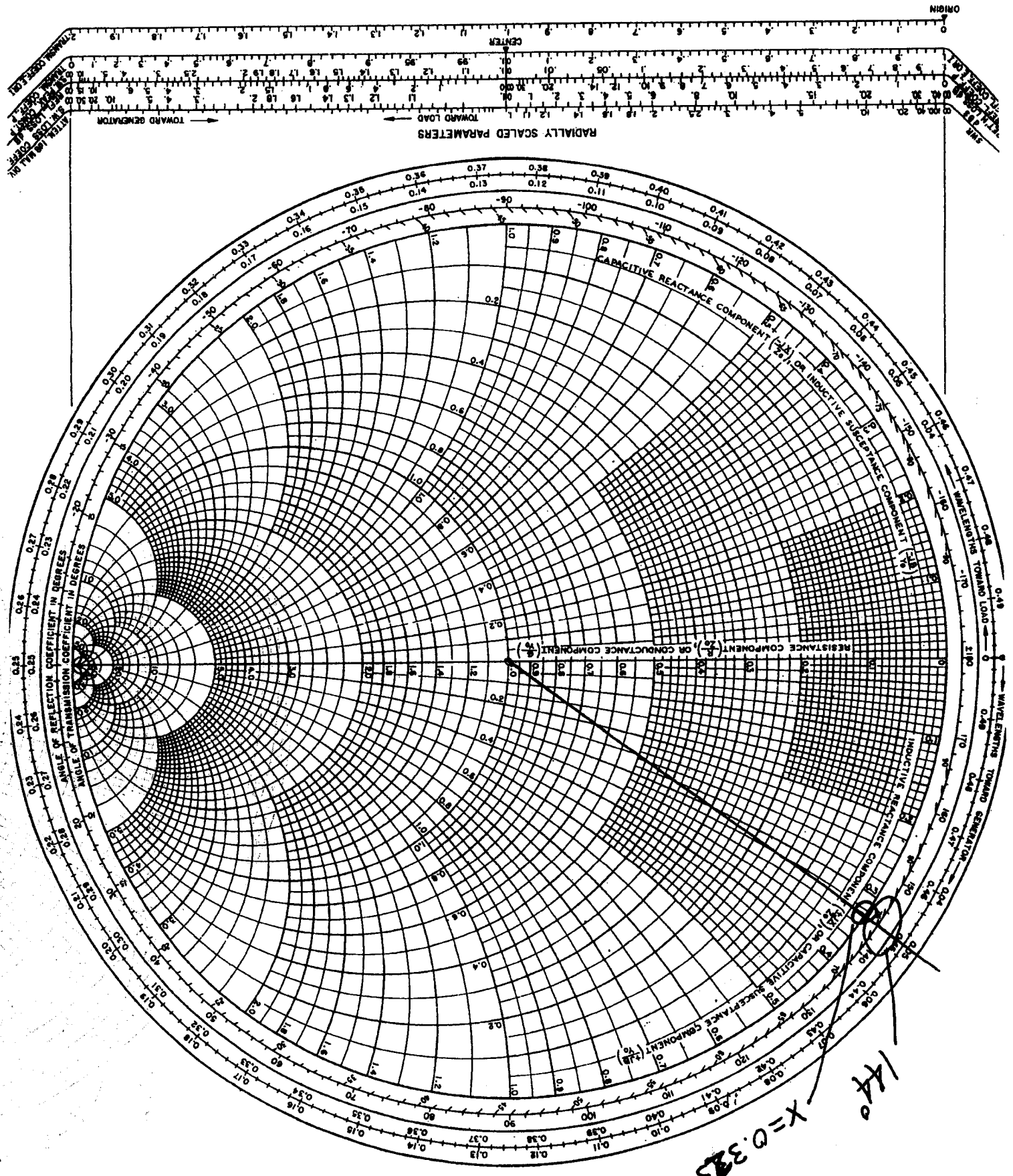
$$P_{avg} = \frac{1}{2} \frac{V_{in}^2}{R_T} = 0.122W$$



IMPEDANCE OR ADMITTANCE COORDINATES

Optional Smith chart

ECE 391 – TRANSMISSION LINES AND ELECTROMAGNETIC WAVES

Winter Term 2004

Midterm II

Name: _____


Solutions

(Last name, first name)

Student ID: xxx-xx-_____

Exam is closed book, closed notes; one sheet (2 pages) of formulas allowed; 50 minutes. Show all your work on the pages provided. No extra pages (use back if necessary). Read each question very carefully. Maximum number of points for each problem is given in parenthesis. Total: 40 points.

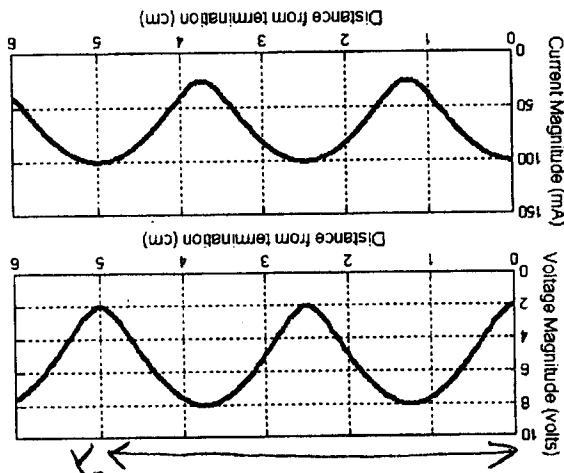1. (14 pts.) A transmission line of unknown characteristic impedance Z_0 is terminated in an unknown load impedance Z_L . The voltage and current standing-wave patterns along the transmission line as function of distance from the termination are shown below.



Answer the following questions. An optional Smith chart is also attached.

(a) What is the standing-wave ratio on the line terminated in the unknown load impedance Z_L ?

$$SWR = \frac{2V}{8V} = \boxed{4}$$

(b) Determine the wavelength on the line.

$$\lambda = 5 \text{ cm}$$

(c) Determine the operating frequency f_0 in Hz if the velocity factor of the transmission line is 50%.

$$V_p = 0.5c = 1.5 \times 10^8 \frac{m}{s}$$

$$f_0 = \frac{v}{\lambda} = \frac{1.5 \times 10^8 \frac{m}{s}}{0.05 m} = \boxed{3 \text{ GHz}}$$

(d) Determine the characteristic impedance of the transmission line.

$$Z_0 = \frac{V_{max}}{I_{max}} = \frac{8V}{100mA} = \boxed{80 \Omega}$$

(e) Determine the magnitude and phase (in degrees) of the reflection coefficient at the termination.

$$|K| = \frac{SWR-1}{SWR+1} = \frac{3}{5} = \boxed{0.6}$$

minimum at termination $\Rightarrow \theta_k = 180^\circ$

or: distance to find maximum = $\frac{\theta_k}{2} = \frac{180^\circ}{2} = 90^\circ$

$$= \frac{1}{4} \lambda \approx 90^\circ \Rightarrow \theta_k = 2 \times 90^\circ = 180^\circ$$

(f) Determine the load impedance in ohms.

Z_T is purely real
 $K = |K|e^{j\theta_k} = -|K| = -0.6 \Rightarrow R_T = Z_0 \frac{1+K}{1-K} = 20 \Omega$

$$\text{or: } Z_T = Z_{min} = \frac{Z_0}{SWR} = \frac{80 \Omega}{4} = 20 \Omega$$

(g) Determine how the voltage standing-wave pattern would change if the load impedance were removed (i.e., for an open-circuited line).

for an open circuit: $V = V_{max,oc}$ at the termination


$$\text{with } V_{max,oc} = 2V_+$$

$$V_+ = \frac{1}{2} (8V + 2V) = 5V$$

$$V_{max,oc} = 2 \times 5V = 10V$$

$$V_{min} = \boxed{0V}$$

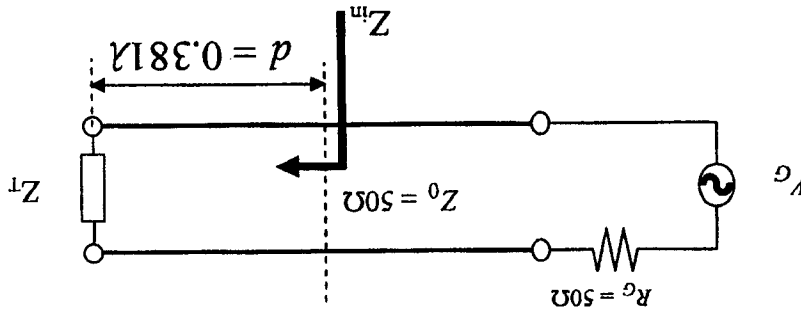2. (17 pts.) A lossless transmission line of characteristic impedance $Z_0 = 50\Omega$ is terminated in the complex impedance $Z_T = R_T + jX_T$. The normalized input impedance $z_{in} = Z_{in}/Z_0$ at distance $d = 0.381\lambda$ from the termination is specified on the attached Smith Chart. Use the attached Smith Chart to solve all of the following problems. Show all your work on the Smith Chart!



(a) From the Smith Chart, find the normalized input impedance $z_{in} = r_{in} + jx_{in}$ and give the input terminating impedance $Z_{in} = R_{in} + jX_{in}$ in ohms.

$$z_{in} = 0.5 - j0.8 \Rightarrow Z_{in} = 3.4 \cdot Z_0 = (25 - j40)\Omega$$

(b) Determine the voltage standing-wave ratio on the line using the Smith chart. (Clearly indicate your solution approach on the Smith chart.) *from Smith chart: SWR ≈ 3.5 (Intersektion with x=0 on right half) or 1/SWR ≈ 0.29 ⇒ SWR = 3.45*

(c) Determine the reflection coefficient (magnitude and phase in degrees) at distance d from the termination using the Smith Chart. *from Smith chart*

$$K_{in}(z=d) = \frac{z_{in} - Z_0}{z_{in} + Z_0} = 0.55 e^{-j94^\circ}$$

Note: For comparison, exact calculation gives $K_{in} = 0.5549 e^{-j93.933^\circ}$

(d) Using the Smith Chart and starting at the location where the input impedance is known

(distance d from the termination), determine the distance to the nearest voltage minimum

$d_{v, \min} / \lambda$ in the direction to the load.
To get to the nearest voltage minimum going forward the load, rotate in counter-clockwise direction until the phase of the reflection coefficient is 180°

\Rightarrow go from 0.119 to $0.5 \Rightarrow \frac{d_{v, \min}}{\lambda} = 0.5 - 0.119 = 0.381$ 0.381

(e) Determine the normalized load impedance $z_T = r_T + jx_T$ at the termination and give the terminating impedance $Z_T = R_T + jX_T$ in ohms.

for $d = 0.381\lambda$, $z_T = z_{\min}$ (from previous problem)

$\Rightarrow \Gamma_T = \Gamma_{\min} = \frac{1}{SWR} \approx 0.29$

and $Z_T = \Gamma_T z_0 \approx 14.5 \Omega$

(f) Using the Smith chart, determine the load impedance if a capacitance with normalized impedance $z_c = -jx_c = -j0.5$ is connected in parallel to impedance $Z_T = R_T + jX_T$. (Show all steps.)

parallel connection \Rightarrow convert to admittance


$Y_T = \frac{1}{Z_T} = \frac{1}{14.5} \approx 0.069$

$Y_c = \frac{1}{Z_c} = \frac{1}{-j2} = j0.5$

$Y_L = Y_c + Y_T = 3.5 + j2$

$\Gamma_L = \frac{1}{2} \approx 2.2 - j0.12$ (from Smith chart)

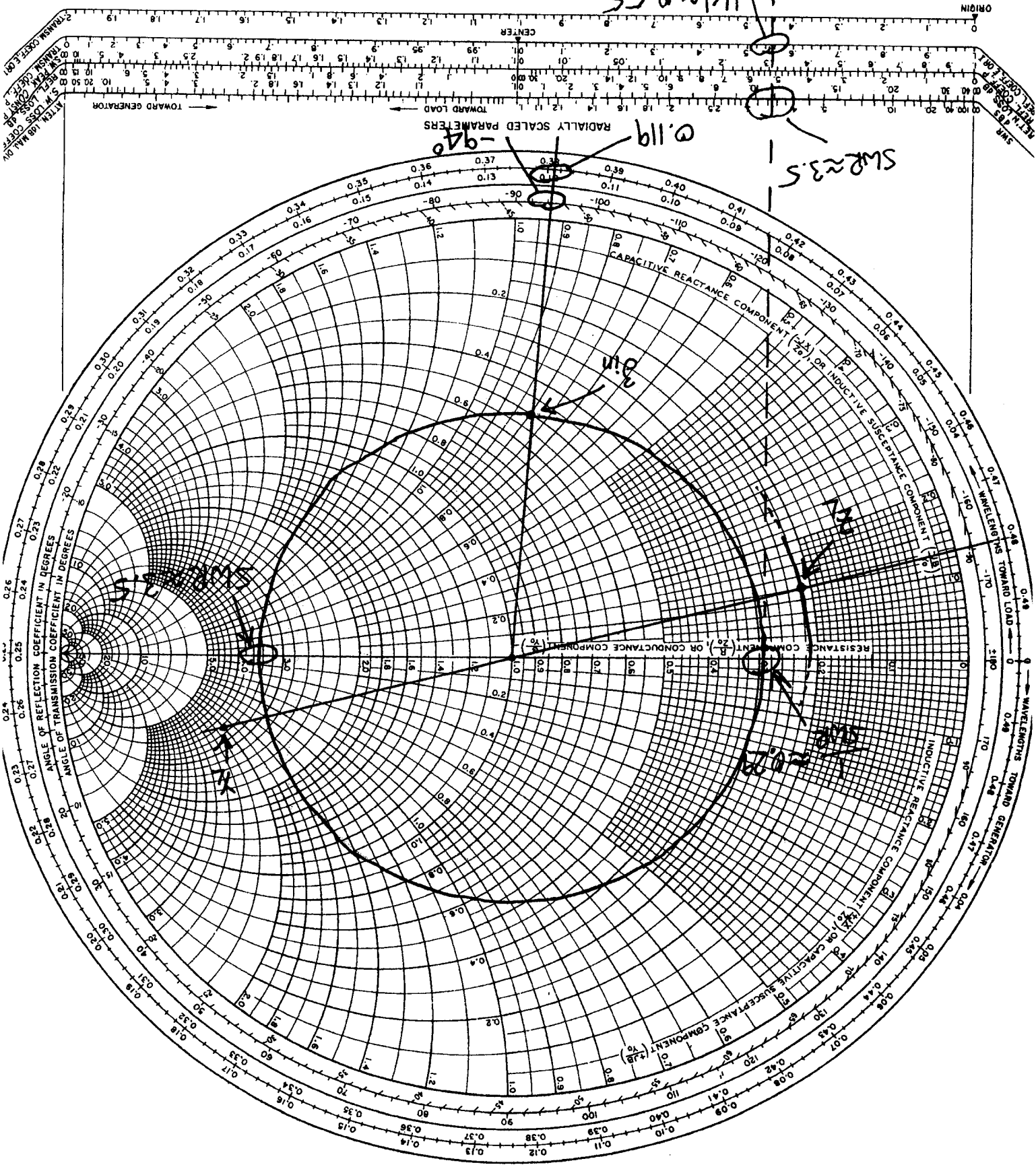
$Z_L = \Gamma_L z_0 \approx (110 - j6) \Omega$



IMPEDANCE OR ADMITTANCE COORDINATES

NAME	TITLE	DWG. NO.	DATE
SMITH CHART FORM 82-BSPR (9-66) KAY ELECTRIC COMPANY, PINE BROOK, N.J. © 1966. PRINTED IN USA.			

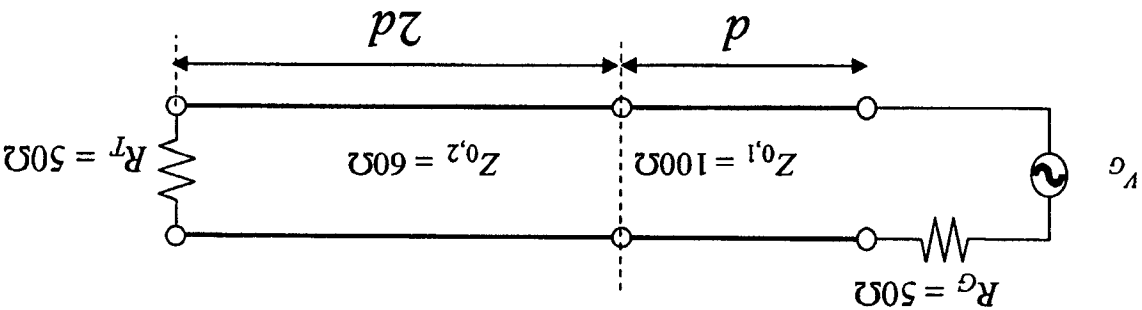3. (9 pts.) A resistive load $R_T = 50\Omega$ is connected through two cascaded transmission line sections to a generator with source resistance $R_G = 50\Omega$ as shown below. At frequency f_0 the line length d corresponds to a quarter wavelength ($d = \lambda/4$).



(a) What is the standing-wave ratio on the left transmission-line segment with characteristic impedance $Z_{01} = 100\Omega$ at operating frequency $f = f_0$ ($d = \lambda/4$)?


for $f = f_0 \Rightarrow d = \lambda/4$ and $2d = \lambda/2$
 \Rightarrow load impedance seen by left line is 50Ω
 $\Rightarrow SWR = \frac{100\Omega}{50\Omega} = 2$ ($= \frac{1}{SWR}$)

(b) What is the average power dissipated in load resistance $R_T = 50\Omega$ if the source has a peak voltage of $10V$ and is operating at frequency $f = f_0$?

input impedance to left line is obtained by $\lambda/4$ transformation
 $Z_{in} = \frac{Z_{01}}{(100\Omega)^2} = \frac{50\Omega}{200\Omega} = 200\Omega$
 $\Rightarrow P_{ave} = \frac{1}{2} \left(\frac{10V}{200\Omega} \right)^2 = \frac{1}{2} \left(\frac{1}{20} \right)^2 = \frac{1}{200}$

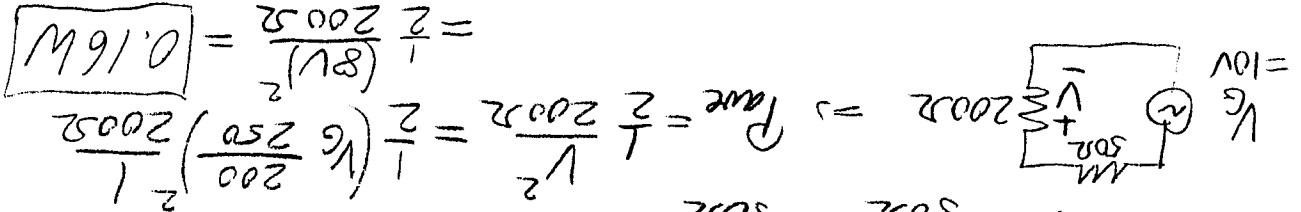(c) What is the average power dissipated in load resistance $R_T = 50\Omega$ if the operating frequency is doubled ($f = 2f_0$)?

for $f = 2f_0$, $d = \frac{\lambda}{2}$ and $2d = \lambda$
 $\Rightarrow Z_{in} = 50\Omega$ and
 $P_{ave} = \frac{1}{2} \frac{(5V)^2}{50\Omega} = 0.25W$



$\Rightarrow P_{ave} = \frac{1}{2} \frac{(8V)^2}{200\Omega} = 0.16W$


ECE 391 - TRANSMISSION LINES AND ELECTROMAGNETIC WAVES

Spring Term 2003
Midterm II

Name: Solutions SSN: xxx-xx-_____ (Last name, first name)

Exam is closed book, closed notes; one sheet (2 pages) of formulas allowed; 50 minutes. Show all your work on the pages provided. No extra pages (use back if necessary). Read each question very carefully. Maximum number of points for each problem is given in parenthesis. Total: 40 points.

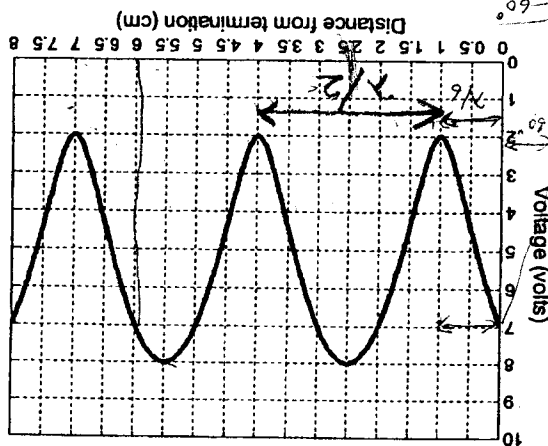1. (13 pts.) A 50Ω transmission line is terminated in an unknown load impedance Z_L . The voltage standing-wave on the transmission line measured in electrical distance from the termination is shown below. Answer the following questions. An optional Smith chart is also attached.



(a) Determine the wavelength on the line.
 $\lambda/2 = 4\text{ cm} - 1\text{ cm} = 3\text{ cm}$

$$\lambda = 6\text{ cm}$$

(b) What is the standing-wave ratio on the line terminated in the unknown load impedance Z_L ?

$$SWR = \frac{V_{max}}{V_{min}} = \frac{8\text{ V}}{2\text{ V}} = 4$$

V_{max}
 $\theta_R = 1560$
 $\theta_L = 3600$ or -600
 $(2.5) \left(\frac{3600}{6} \right)$

$$60 \cdot 2\pi \cdot \frac{360}{360} = \frac{6}{3} = 2$$

$$P_{\text{loss}} = \frac{1}{2} |V_m|^2 (1 - |k|^2) = \frac{1}{2} (5V)^2 (1 - 0.36) = \boxed{160 \text{ mW}}$$

(f) What is the average power (in watts) dissipated in the terminating impedance Z_T ?

Or: $V_{\text{max}} + V_{\text{min}} = V_+ (1 + |k|) + V_- (1 - |k|) = 2V_+$
 $V_+ = \frac{V_{\text{max}} + V_{\text{min}}}{2} = \frac{8V + 2V}{2} = 5V$

$$V_+ (1 + |k|) = 8V = V_{\text{max}} \Rightarrow V_+ = \frac{8V}{1 + |k|} = \frac{8V}{1.6} = 5V$$

(e) Determine the voltage amplitude V_+ of the outgoing wave.

$$\Rightarrow Z_T = 20j \Rightarrow \boxed{(42 - j68.5) \Omega}$$

arbitrary complex termination

or, from Smith chart: $\Gamma_T \approx 0.84 - j1.37$

$$Z_T = 50 \frac{1 + \Gamma_T}{1 - \Gamma_T} = 50 \frac{1 + (0.84 - j1.37)}{1 - (0.84 - j1.37)}$$

(d) Determine the load impedance in ohms.

or from Smith chart: draw SWR = 4 circle from V_{min} location, go $\frac{1}{2} \lambda = 0.1667 \lambda$ towards load $\Rightarrow \phi = -60^\circ$

$$|k| = \frac{Z_T - Z_0}{Z_T + Z_0}$$

Phase calculation: distance to 1st voltage minimum = $l_{\text{min}} = \frac{\lambda}{2} \sqrt{60^\circ} = 300^\circ \Rightarrow \phi = -60^\circ$


$$|k| = \frac{\text{SWR} - 1}{\text{SWR} + 1} = \frac{4 - 1}{4 + 1} = \frac{3}{5} = \boxed{0.6}$$

(c) Determine the magnitude and phase (in degrees) of the reflection coefficient at the termination.

$$V_{\text{min}} = -60^\circ \Rightarrow \phi = -60^\circ$$

Optional Smith chart for problem 1

IMPEDANCE OR ADMITTANCE COORDINATES

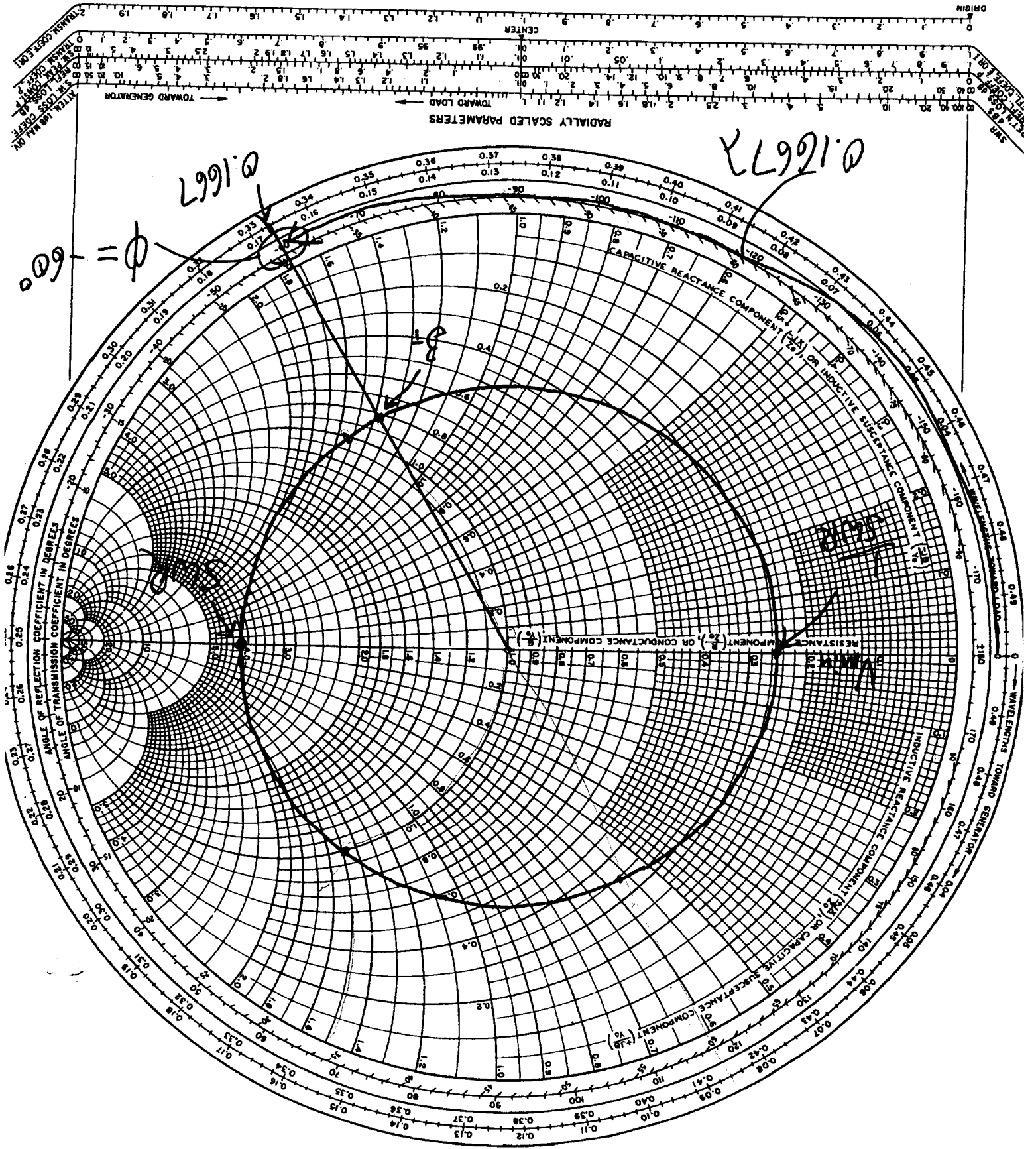

2. (17 pts.) A lossless transmission line of characteristic impedance $Z_0 = 100\Omega$ is terminated in the complex impedance $Z_T = R_T + jX_T$. The normalized terminating impedance $z_T = Z_T/Z_0$ is specified on the attached Smith Chart. Use the attached Smith Chart to solve all of the following problems. Show all your work on the Smith Chart!

(a) From the Smith Chart, find the normalized terminating impedance $z_T = r + jx$ and give the terminating impedance $Z_T = R_T + jX_T$ in ohms.

$$z_T = 0.5 - j0.7 \Rightarrow Z_T = 50 - j70 \Omega$$

(b) Determine the voltage standing-wave ratio on the line using the Smith chart. (Clearly indicate your solution approach on the Smith chart.)

$$SWR \approx 3.2$$

(c) Determine the reflection coefficient (magnitude and phase in degrees) at the termination using the Smith Chart.

$$|K| \approx 0.52$$

$$\theta_K \approx -101^\circ$$

(d) Determine the distance to the nearest voltage minimum $d_{v,min}/\lambda$ from the termination using the Smith Chart.

$$d_{v,min}/\lambda \approx 0.5 - 0.39 = 0.11$$

Now, the complex termination is to be matched to the transmission line using a variable series-connected capacitor.

(e) Determine the position d/λ at which the capacitor is to be connected in series to the transmission line (using the Smith chart).

go on SWR = 3.2 ($|V| = 0.5$) circle
 in clockwise direction until you intersect
 with $r = 1$ circle. Look for inductive SWR has

$$\frac{d}{\lambda} = (0.5 - 0.39) + 0.18 = 0.278$$

(f) Determine the capacitance value C to achieve a match at the design frequency $f = 100$ MHz.

$$S_{in} = 1 + j1.22$$

$$Z_{in} = (100 + j122) \Omega$$


to compensate with a series-connected capacitor, we need to have

$$\frac{1}{j\omega C} = -j122 \Omega$$

$$C = \frac{1}{\omega \cdot 122 \Omega} = \frac{1}{2\pi \cdot 100 \cdot 10^6 \cdot 122} \approx 13 \text{ pF}$$

$$\approx 13 \text{ pF}$$

$|K| \approx 0.52$

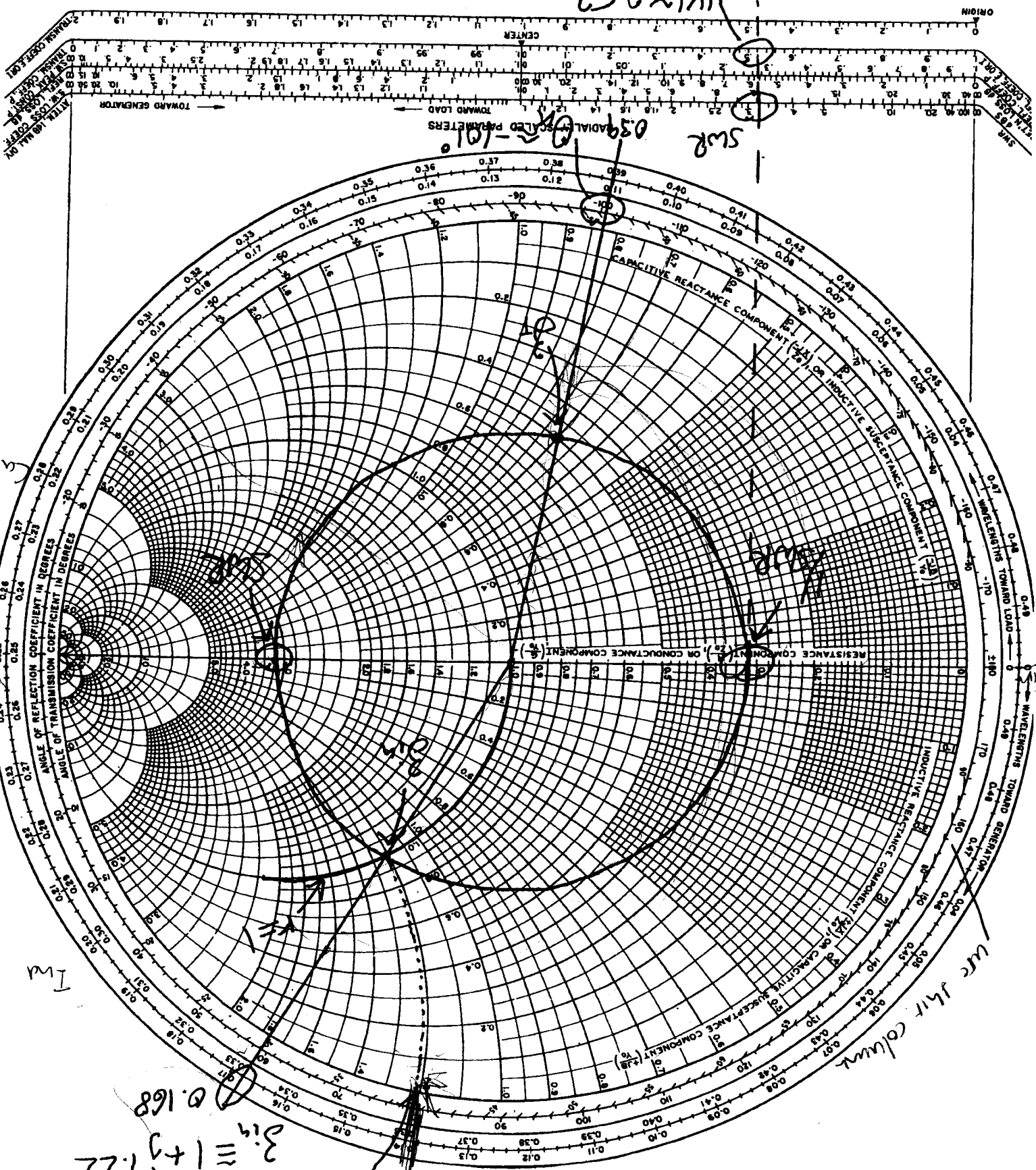


IMPEDANCE OR ADMITTANCE COORDINATES

$X \approx 1.22$

Smith chart for problem 2

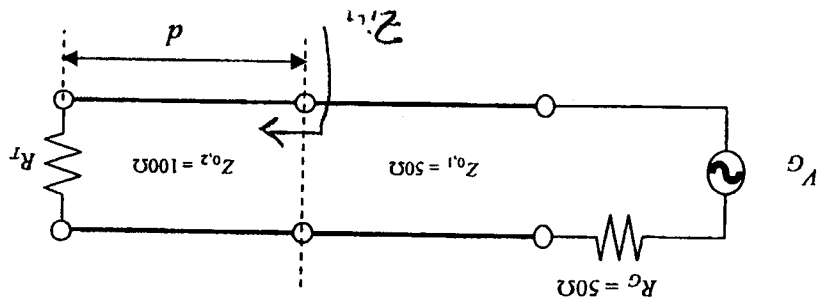3. (10 pts.) An unknown resistive load R_T is connected through a transmission line section of length d and characteristic impedance $Z_{0,2} = 100\Omega$ to a $Z_{0,1} = 50\Omega$ transmission line, as shown below. At frequency f_0 the line length d corresponds to half a wavelength ($d = \lambda/2$).



(a) What is the length of the line if $f = f_0 = 200$ MHz and the effective dielectric constant of the transmission line is $\epsilon_{r,eff} = 4$?

$$\lambda = \frac{f}{V_p} = \frac{f}{\frac{c}{\sqrt{\epsilon_{r,eff}}}} = \frac{1}{\sqrt{4}} \frac{f}{c} = 75\text{cm}$$

$$\Rightarrow d = \lambda/2 = 37.5\text{cm}$$

(b) Determine R_T if at $f = f_0$ the standing-wave ratio on the 50Ω line is $SWR = 1$.

$$\text{for } d = \lambda/2, Z_{in} = R_T$$

Since $SWR = 1$, the line is matched $\Rightarrow R_T = Z_0 = 50\Omega$

(c) What is the standing-wave ratio on the 50Ω line if the frequency is halved ($f = f_0/2$)?

$$\text{for } f = f_0/2, d = \lambda/4$$

$$Z_{in} = \frac{Z_{0,2}^2}{R_T} = \frac{(100\Omega)^2}{50\Omega} = 200\Omega = Z_{max} \text{ on line 1}$$

$$\Rightarrow SWR = \frac{200\Omega}{50\Omega} = 4$$

(d) What is the standing-wave ratio on the 50Ω line at $f = f_0/2$ if the load resistor R_T is replaced with a capacitor $C = 31.8$ pF and the frequency is $f = f_0/2 = 100$ MHz?

purely reactive (capacitive) termination has

$$\Rightarrow SWR = \infty$$

ECE 391 - TRANSMISSION LINES AND ELECTROMAGNETIC WAVES

Winter Term 2002

Midterm II


Name: _____

(Last name, first name)

SSN: xxx-xx-_____

Exam is closed book, closed notes, one sheet (2 pages) of formulas allowed; 50 minutes. Show all your work on the pages provided. No extra pages (use back if necessary). Read each question very carefully. Maximum number of points for each problem is given in parenthesis. Total: 40 points.

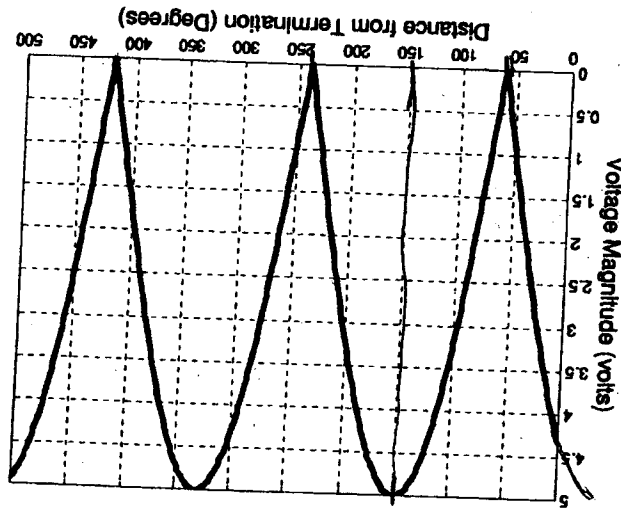1. (10 pts.) A 100Ω transmission line is terminated in an unknown load impedance Z_L . The voltage standing-wave on the transmission line measured in electrical distance from the termination is shown below.



$\theta/2 = 150$
 $\Rightarrow \theta = 300$

$\theta/2 = 150$
 $\theta_k = 360$
 $500 - 150 = 350$

2/2 (a) What is the standing-wave ratio on the line terminated in the unknown load impedance Z_L ?

$$SWR = \frac{|V_{max}|}{|V_{min}|} = \frac{5V}{0V} = \infty$$

2/2 (b) Determine the voltage amplitude V_m^* of the incident wave.

$$V_m^* = \frac{2}{|V_{max}| + |V_{min}|} = 2.5V$$

3/3 (c) Determine the reflection coefficient at the termination (magnitude and phase).

$$SWR = \infty \Rightarrow |K| = \frac{SWR-1}{SWR+1} = 1$$

Voltage minimum shifted from termination by

$$\frac{\theta_k}{2} + 90^\circ = 60^\circ \Rightarrow \theta_k = -60^\circ$$

$$\phi = \theta_k - 2\beta z$$

$$\theta_k = 2\beta z \pm \pi$$

or find voltage maximum occur at

$$\frac{\theta_k}{2} = 150^\circ \Rightarrow \theta_k = 300^\circ = -60^\circ$$

3/3 (d) Determine the load impedance Z_L in ohms. (An optional Smith Chart is attached at the end.)

from Smith chart: $\beta l = -j1.73$

$$\Rightarrow Z_L = \beta l * Z_0 = -j1.73 \Omega$$

calculated:

$$Z_L = Z_0 \frac{1+k}{1-k} = Z_0 \frac{1+e^{-j60^\circ}}{1-e^{-j60^\circ}} = -j1.732 \Omega$$

2. (18 pts.) A lossless transmission line of characteristic impedance $Z_0 = 100\Omega$ is terminated in an unknown complex impedance $Z_m(d) = Z_0 \left[\frac{1 + \Gamma_m e^{-j2\beta d}}{1 - \Gamma_m e^{-j2\beta d}} \right]$. The normalized input impedance $Z_m(d)/Z_0$ at distance $d = 1.2\lambda$ from the termination is specified on the attached Smith Chart. Use the attached Smith Chart to solve all of the following problems. Show all your work on the Smith Chart!

2/2(a) Determine the input impedance $Z_m(d) = R + jX$ in ohms.

$$\Rightarrow Z_m = (50 - j60)\Omega$$

$$\Gamma_m = 0.5 - j0.6 = \Gamma_m / Z_0$$

2/2(b) Determine the corresponding input admittance in siemens.

from Smith chart

$$Y_m \approx 0.82 + j0.98$$

$$\Rightarrow Y_m = \frac{1}{Z_m} = \frac{1}{(8.2 + j9.8) \cdot 10^{-3} \Omega} = (8.2 + j9.8) \cdot 10^{-3} S$$

4/4 (c) Determine the reflection coefficient (magnitude and phase in degrees) at distance d from the termination.

$$|\Gamma| \approx 0.48$$

$$\theta_{\Gamma} \approx -108^\circ$$

from Smith chart

2/2 (d) Determine the voltage standing-wave ratio on the line.

$$VSWR \approx 2.85 \text{ (from Smith chart)}$$


4/4 (e) Determine the terminating impedance $Z_T = R_T + jX_T$ in ohms.

$$\frac{\lambda}{4} = 1.2 \Rightarrow 0.2 \Rightarrow \text{go from } 0.10 \text{ to } 0.30 \text{ (ccw)}$$

$$\Gamma_T \approx 1.7 + j1.25$$

$$\Rightarrow Z_T = (170 + j125)\Omega$$

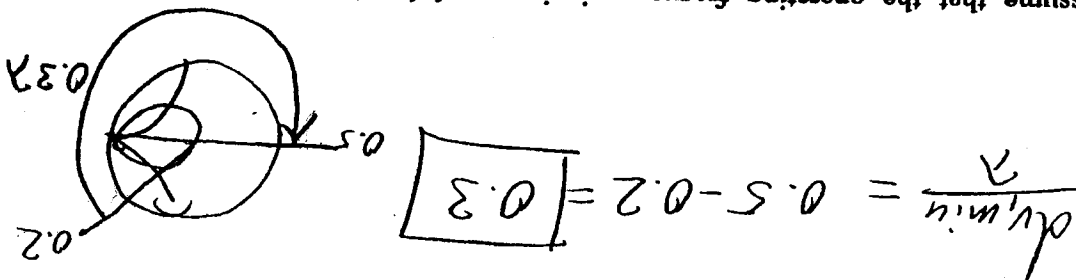2/2 (f) Determine the distance to the nearest voltage minimum d_{vmin} from the termination.



$$d_{vmin} = 0.5 - 0.2 = 0.3$$

2/2 (g) Now, assume that the operating frequency is increased by 20% and the terminating impedance remains unchanged. Determine the new input impedance at distance d from the termination. Hint: the physical distance d remains unchanged.

$$f_{new} = f_{old} * 1.2 \text{ (20\% increase)}$$

$$\lambda_{new} = \lambda_{old} / 1.2 = 0.8333 \lambda_{old} \quad \frac{1}{1.2} = 0.8333$$

$$\frac{d}{\lambda_{new}} = \frac{d}{\lambda_{old}} * 1.2 = 1.2 * 1.2 = 1.44 \approx 0.44$$

\Rightarrow rotate from z_T clockwise by 0.44

$$0.44 + 0.2 = 0.64 \approx 0.14$$

$$z_{in, new} \approx 0.73 + j0.9$$


$$z_{in, new} \approx (73 + j90) \Omega$$

Problem #2


IMPEDANCE OR ADMITTANCE COORDINATES

1.25 0.18

0.3

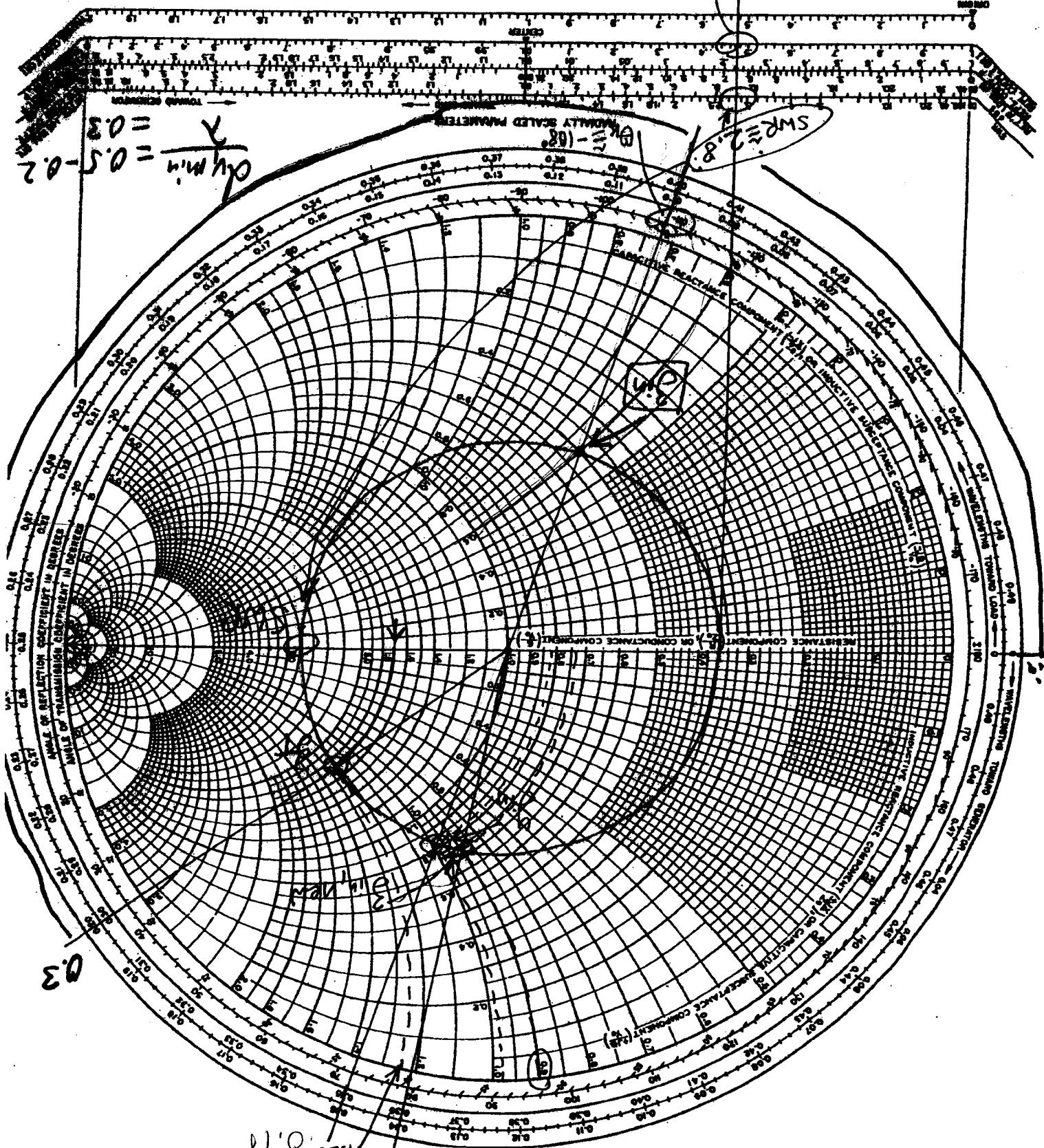

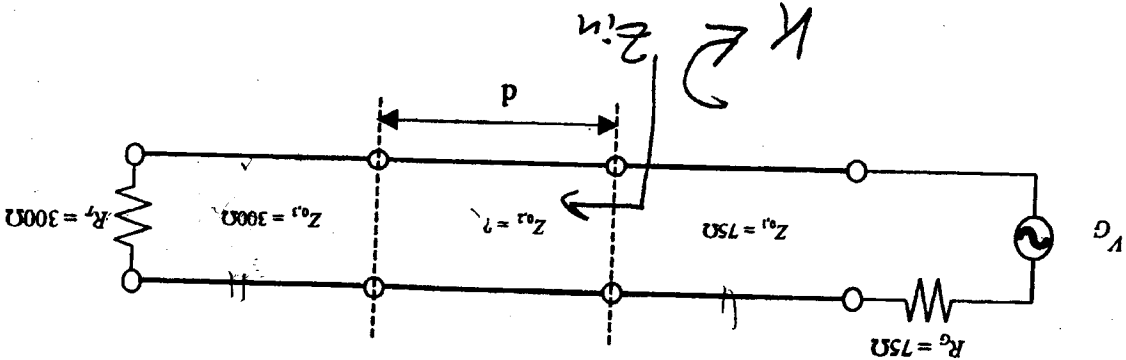3. (12 pts.) A 300Ω load is to be matched to a 75Ω lossless coaxial cable through a section of transmission line of undetermined characteristic impedance Z_{02} and length d , as shown below.



3/3 (a) Determine the characteristic impedance Z_{02} of the connecting line section. Use quarter-wave transformer to match

$$Z_{02} = \sqrt{Z_{01} * Z_{03}} = \sqrt{75\Omega * 300\Omega} = 150\Omega$$

3/3 (b) For an operating frequency of $f = 125$ MHz, determine the shortest length d of the connecting line section to achieve a match. Assume a propagation velocity of $v_p = 25$ cm/nsec.

$$\lambda = \frac{v_p}{f} = \frac{2.5 \times 10^8 \text{ m/s}}{125 \times 10^6 \text{ Hz}} = 2 \text{ m}$$

$$d = \frac{\lambda}{4} = \frac{50 \text{ cm}}{4} = 12.5 \text{ cm}$$

3/3 (c) What is the standing-wave ratio on the line connected to the generator if the operating frequency is doubled ($f = 250$ MHz)?

for $f = 250 \text{ MHz}$ $\lambda = 1 \text{ m}$

$$\Rightarrow \frac{\lambda}{d} = \frac{1}{12.5} = 0.08$$

$$\Rightarrow Z_{in} = 300\Omega$$


$$|K| = \frac{Z_{in} - Z_{01}}{Z_{in} + Z_{01}} = \frac{300 - 75}{300 + 75} = 0.6$$

$$SWR = \frac{1 + |K|}{1 - |K|} = \frac{1 + 0.6}{1 - 0.6} = 4$$

OR $SWR = \frac{Z_{max}}{Z_0} = \frac{300\Omega}{75\Omega} = 4$

half-wave transformer

3/3 (d) Now the connecting line with characteristic impedance Z_{02} is lossy, resulting in a mismatch on the line connected to the generator at $f = 125 \text{ MHz}$. The standing-wave ratio on the line connected to the generator is found as $SWR = 1.5$. Determine the attenuation constant of the connecting lossy line. (An optional Smith chart is attached at the end.) Note: You may want to work on this problem last.

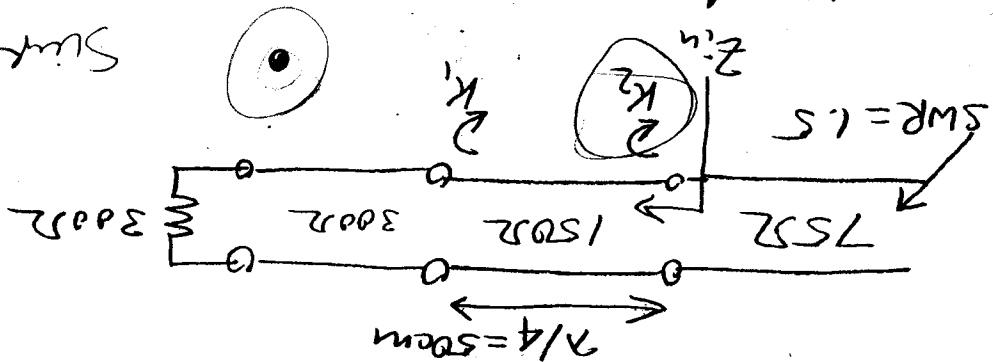


Without loss: $Z_{in} = 75 \Omega$

With loss in $\lambda/4$ section: $Z_{in} > 75 \Omega$ (close to $Z_{02} = 150 \Omega$)

\Rightarrow from $SWR = 1.5$ follows $Z_{in} = Z_{max} = SWR \cdot Z_0 = 450 \Omega$

$= 112.5 \Omega$

w/o loss: $|k_1| = |k_2|$
with loss: $|k_2| = |k_1| e^{-2\alpha d}$

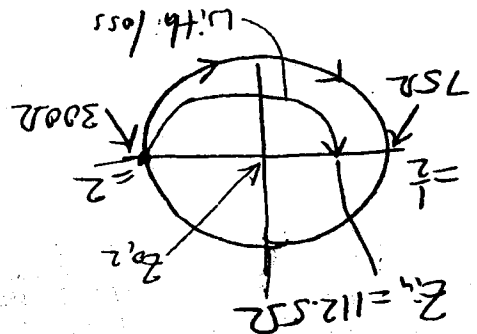


calculated or from Smith chart:

$|k_1| = \left| \frac{300 - 150}{300 + 150} \right| = \frac{1}{3}$

$|k_2| = \left| \frac{112.5 - 150}{112.5 + 150} \right| = 0.143$

$\Rightarrow \alpha = \frac{1}{2d} \ln \frac{|k_1|}{|k_2|}$

$= 0.845 \frac{Np}{m}$

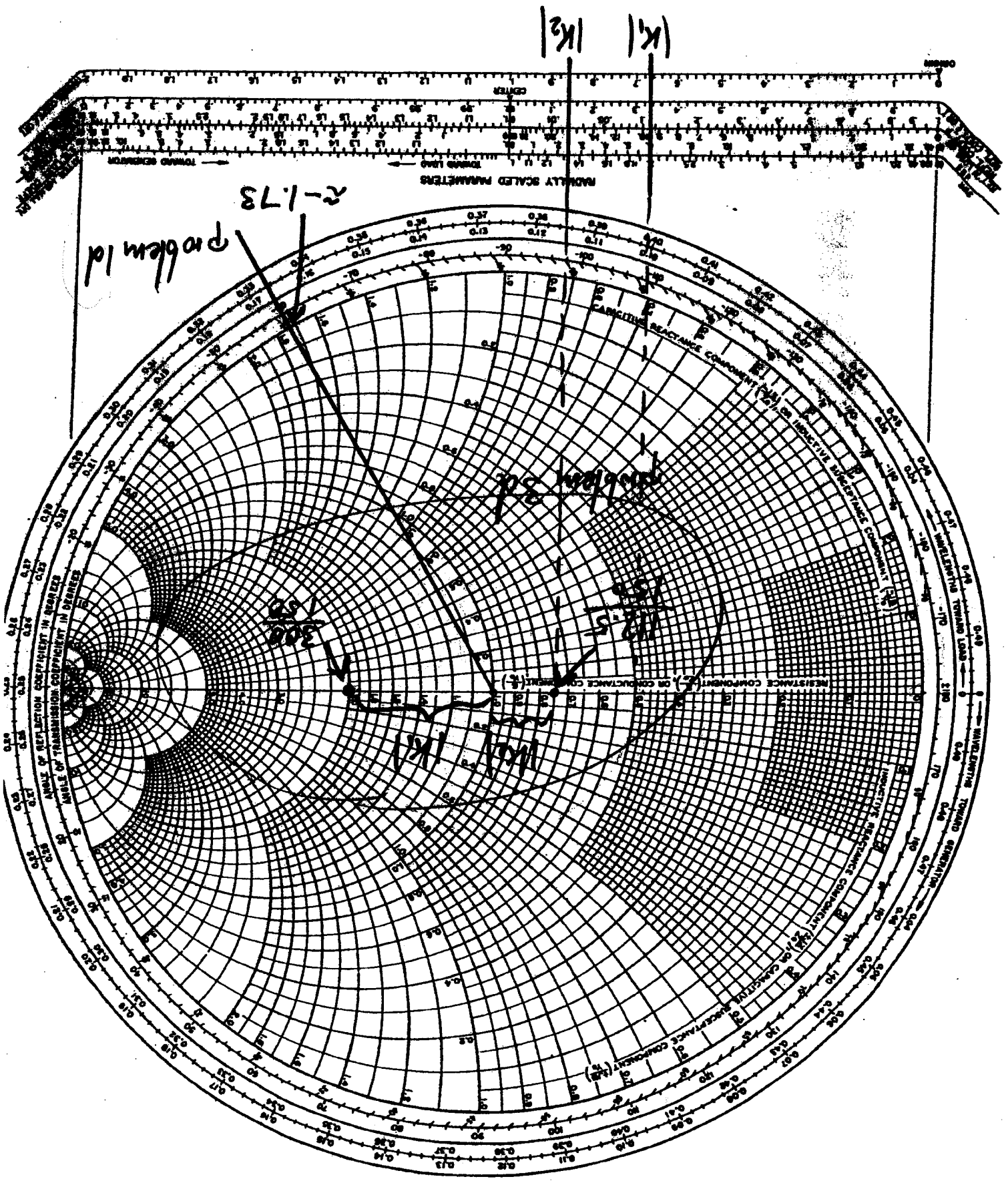

IMPEDANCE OR ADMITTANCE COORDINATES

Optional Smith chart for problems #1 and #3

Stub matching, The new and improved zane method.

RULES:

LENGTH and DISTANCE of stub must be positive.
 Distance in the direction of the generator is always positive (clockwise).
 Always measure distance going in the direction of the generator.
 Distance must be measured in lambda's.
 Always use outer most ring on chart when measuring lambda.
 Smiling is a must when solving.

PROCEDURE:

1. normalize
2. plot on smith chart
3. draw radial load line
4. draw $k = \text{circle}$
5. if shunt, change to admittance
6. if shunt, draw new load line
7. locate intersections of $r=1$ ($g=1$) circle and $k = \text{circle}$
- 8a. for inductive solution choose point in capacitive region,
- 8b. for capacitive solution choose point in inductive region.
9. draw stub line from $1+j0$ to chosen point
10. measure distance in lambda from the load line to the stub line (clockwise direction)
11. record distance as the distance from load to stub
12. find imaginary part of the stub line at $r=1$ ($g=1$)
13. plot the inverse of the imaginary part on the $g=0$ circle (should be on other side of horizontal axis)
14. this new line is the length line
15. The following is how to get the length of the stub
 - 15a. for open stub in shunt configuration: measure distance from left side to the length line
 - 15b. for shorted stub in shunt configuration: measure distance from right side to the length line
 - 15c. for open stub in series configuration: measure distance from right side to the length line
 - 15d. for shorted stub in series configuration: measure distance from left side to the length line

References:

<http://classes.engr.orst.edu/eecs/winter04/ece391>
<http://www.ee.surrey.ac.uk/Personal/D.Jefferies/jefferies-stub.html>
 ver. 1.0.1e (c) 2004 Zane Kenney, Personal reproduction allowed